

TFE4152 - Lecture 9

Current mirrors and Amplifiers

Source

Week	Book	Monday	Book	Friday
34		Introduction, what are we going to do WH 1 , WH 15 in this course. Why do you need it?		Manufacturing of integrated circuits
35	CJM 1.1	pn Junctions	CJM 1.2 WH 1.3, 2.1-2.4	Mosfet transistors
36	CJM 1.2 WH 1.3, 2.1-2.4	Mosfet transistors	CJM 1.3 - 1.6	Modeling and passive devices
37		Guest Lecture - Sony	CJM 3.1, 3.5, 3.6	Current mirrors
38	CJM 3.2, 3.3,3.4 3.7	Amplifiers	CJM, CJM 2 WH 1.5	SPICE simulation and layout
39		Verilog		Verilog
40	WH 1.4 WH 2.5	CMOS Logic	WH 3	Speed
41	WH 4	Power	WH 5	Wires
42	WH 6	Scaling Reliability and Variability	WH 8	Gates
43	WH 9	Sequencing	WH 10	Datapaths - Adders
44	WH 10	Datapaths - Multipliers, Counters	WH 11	Memories
45	WH 12	Packaging	WH 14	Test
46		Guest lecture - Nordic Semiconductor		
47	CJM	Recap of CJM	WH	Recap of WH

Goal for today

Current mirrors

Amplifiers

liraata

Process variations - Correction


Wrong

Assume strong inversion and active $V_{eff} = \sqrt{2\mu_p C_{ox} \frac{W}{L} I_1}$

Correct


Assume strong inversion and active $V_{eff} = \sqrt{\frac{2}{\mu_p C_{ox} \frac{W}{L}} I_1}$

Large signal vs small signal

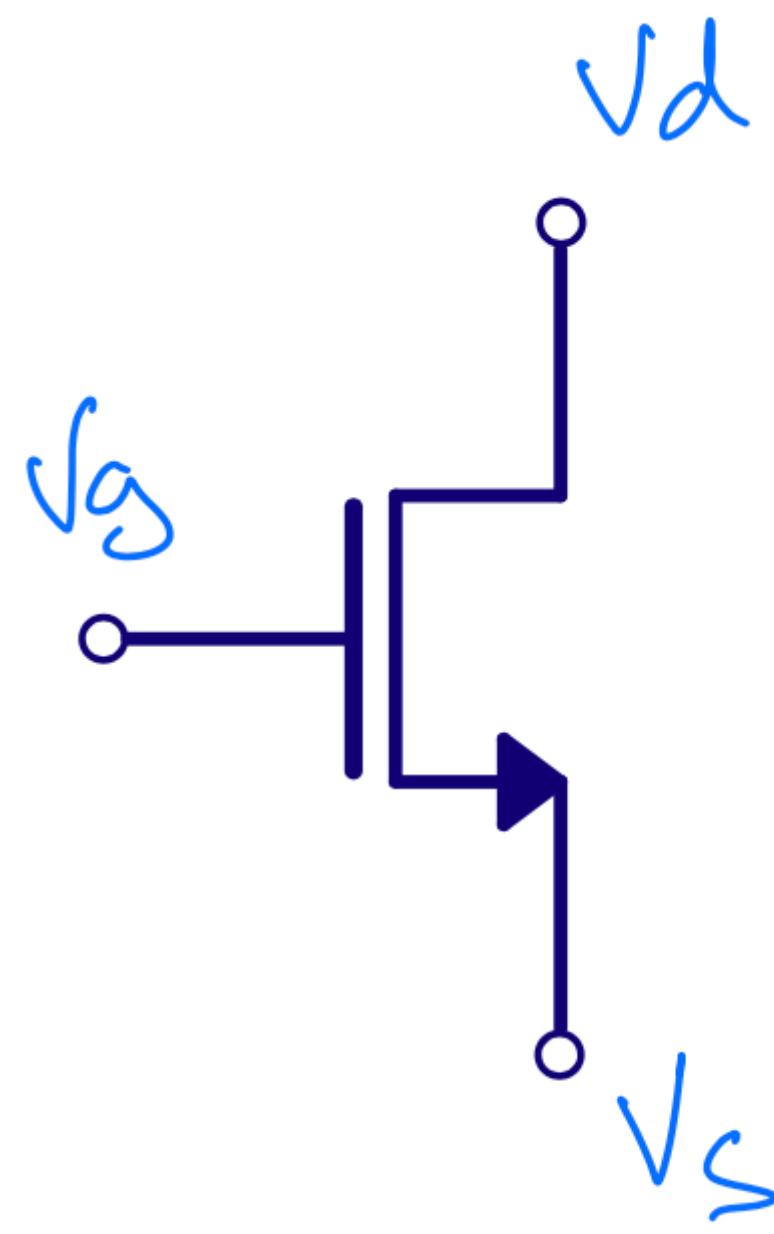


Large signal


Carsten Wulf 2021

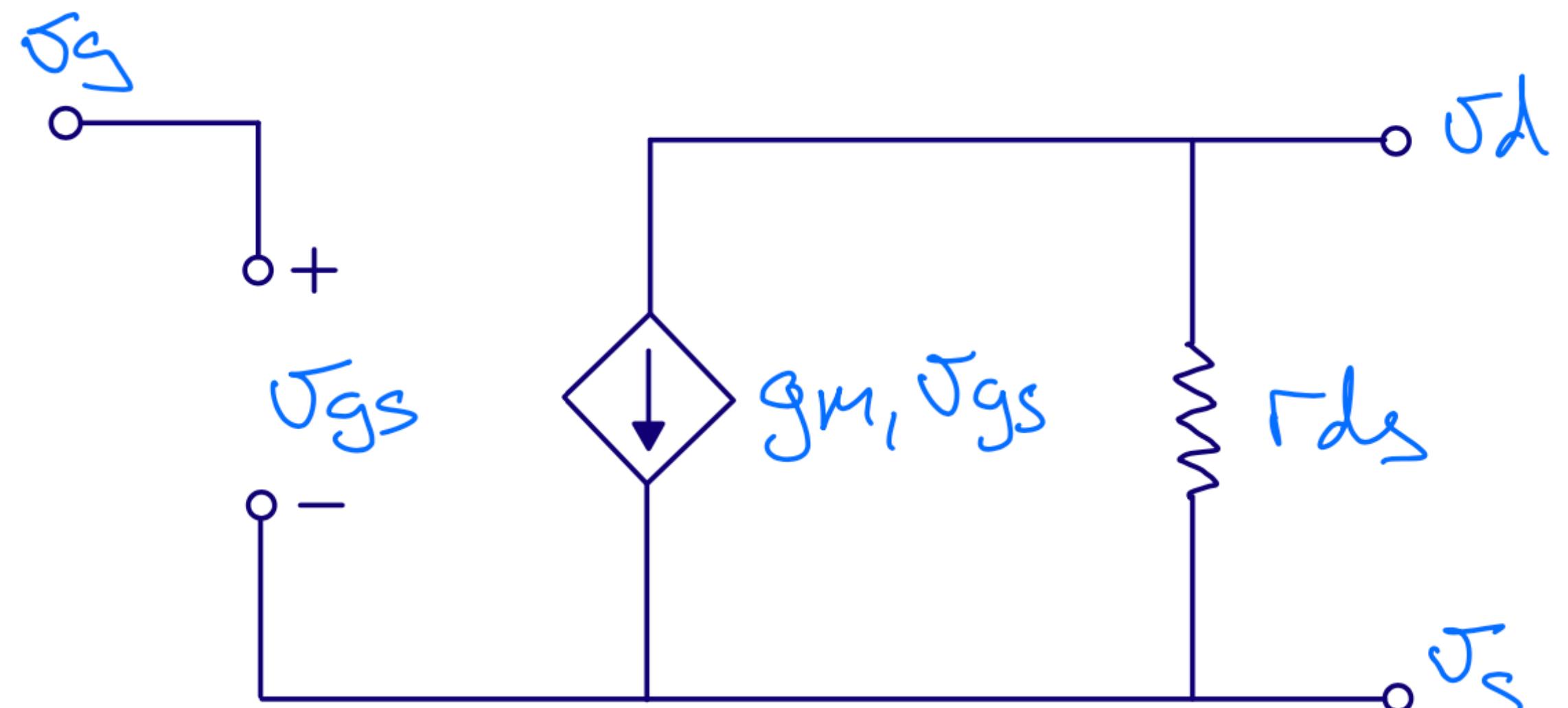


Small signal

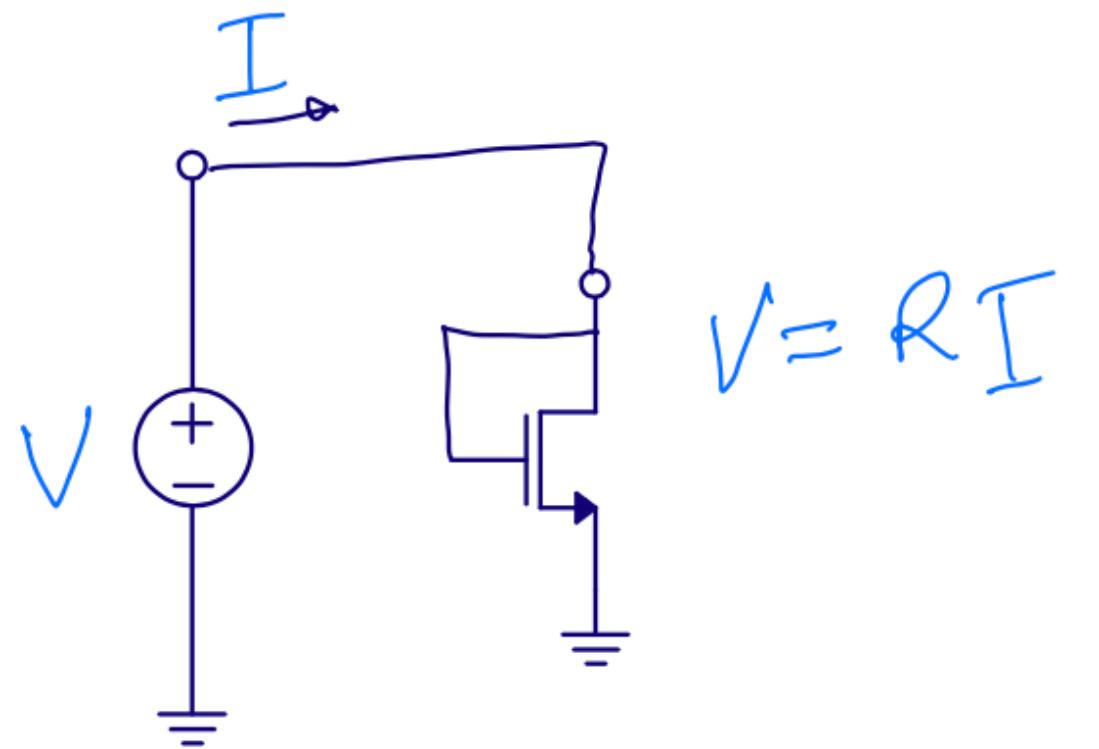


$$I \neq i$$

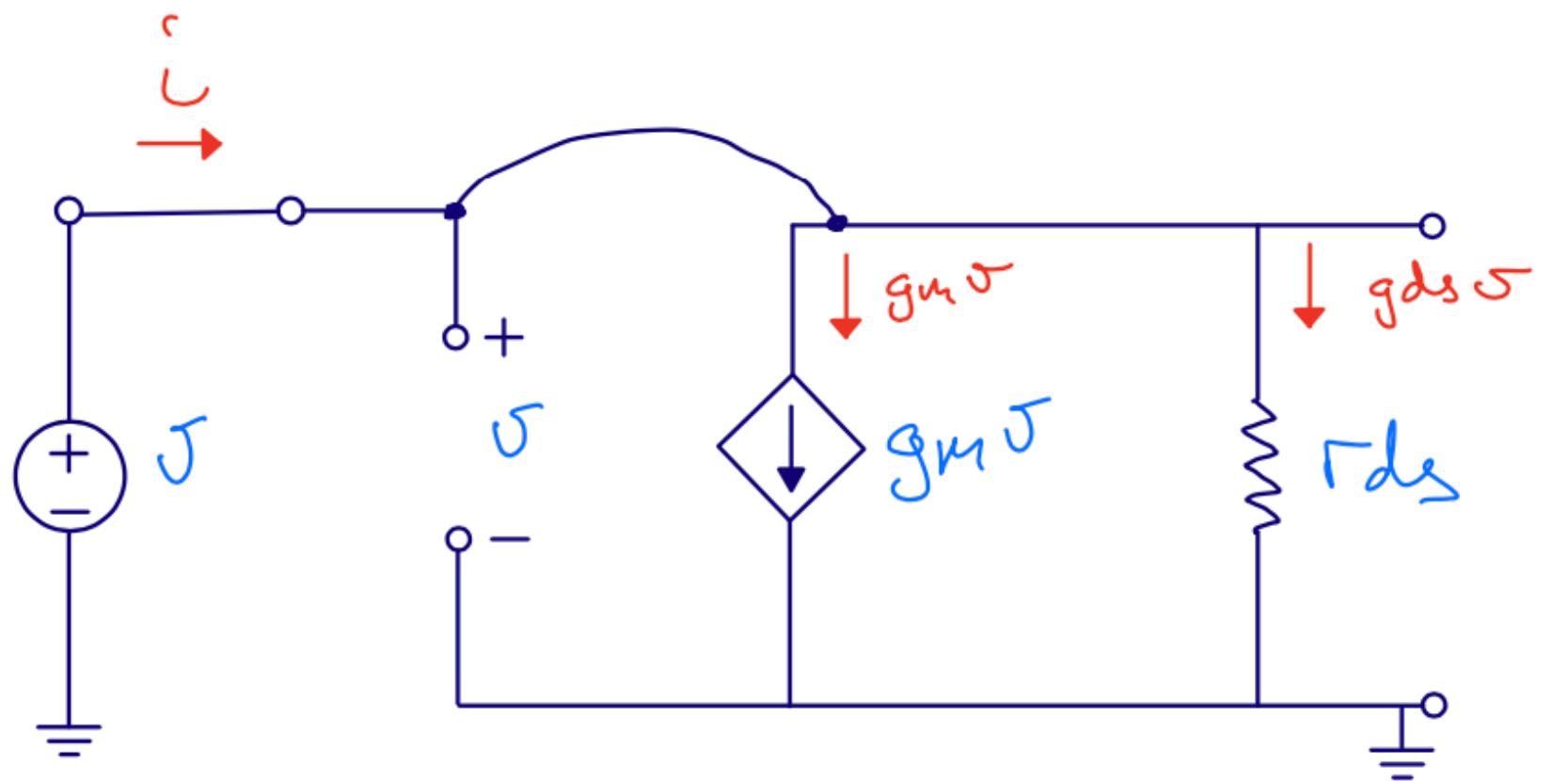

$$V \neq v$$



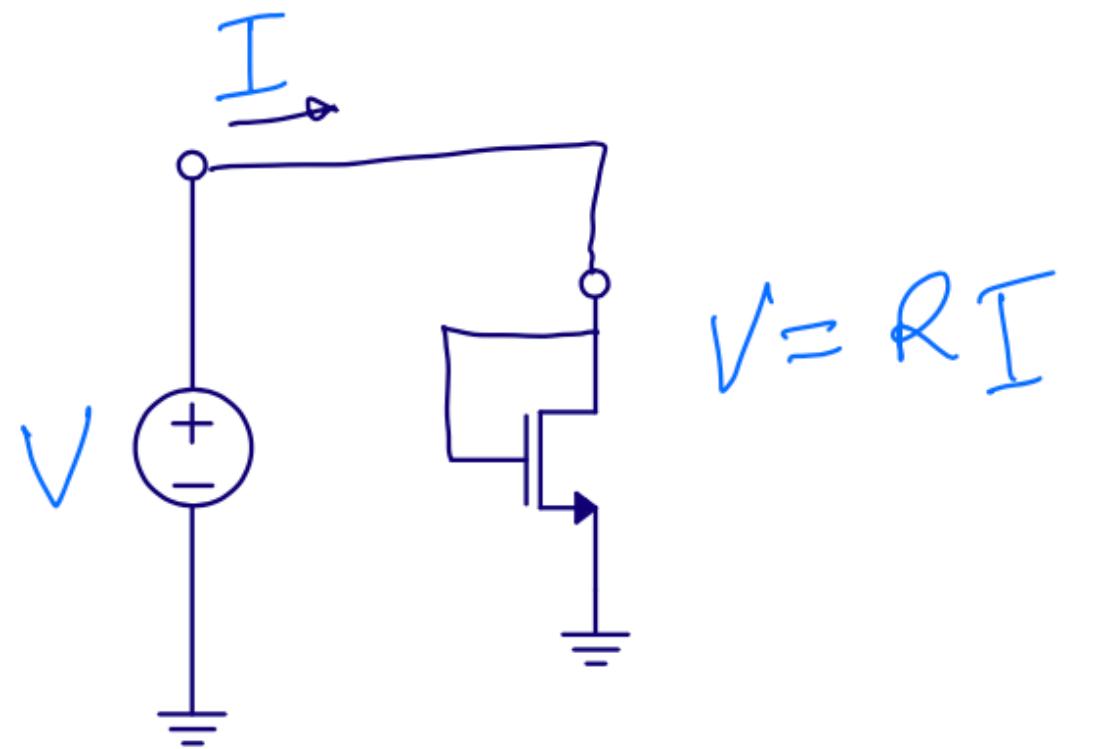


$$I = I_{bias} + i$$

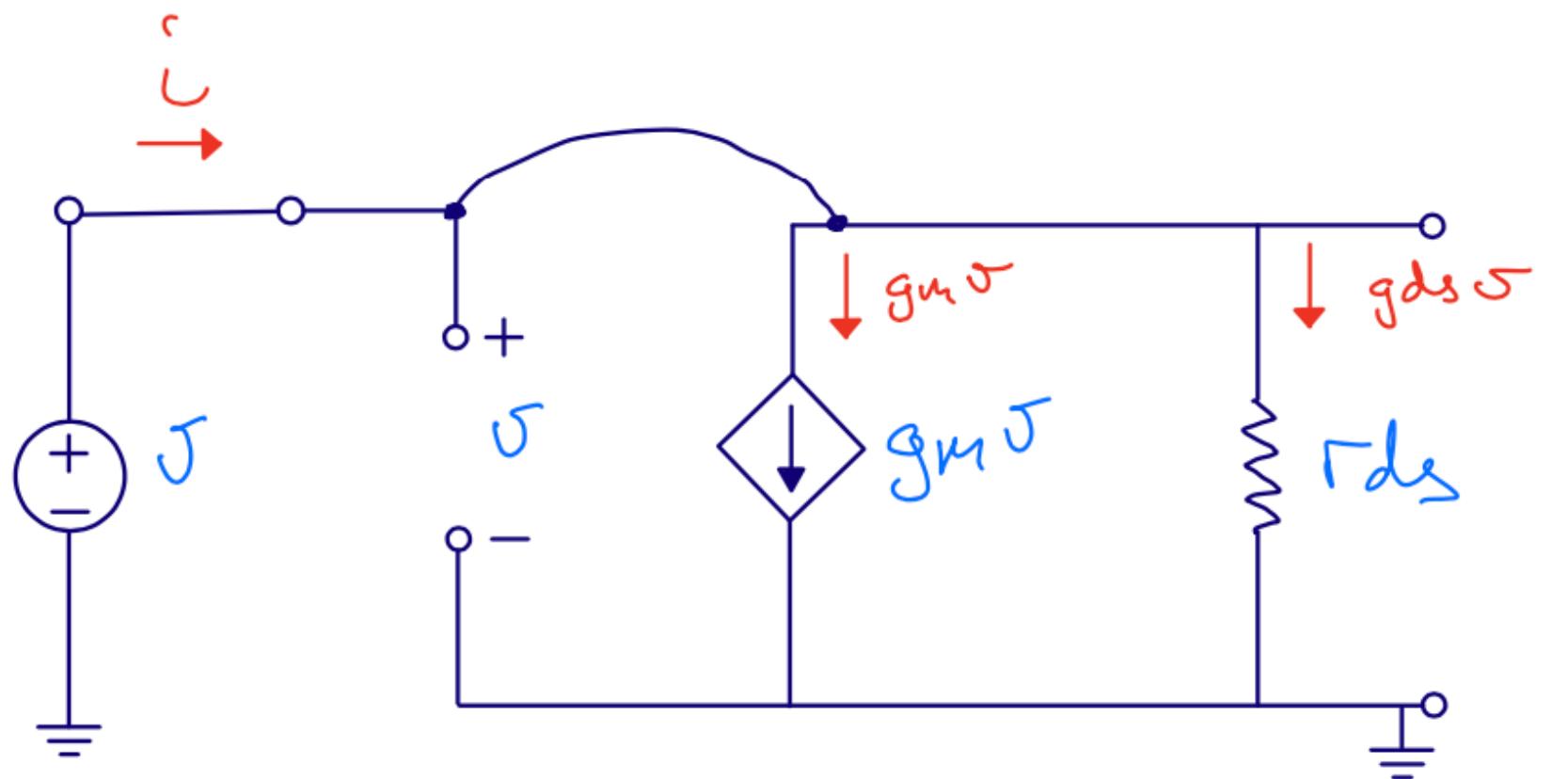


$$V = V_{bias} + v$$

Current Mirror

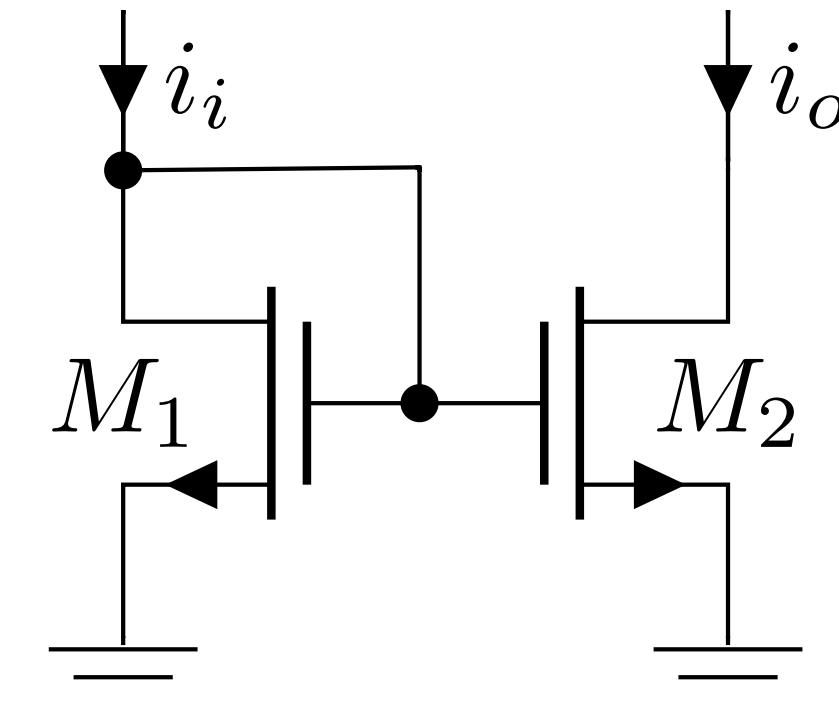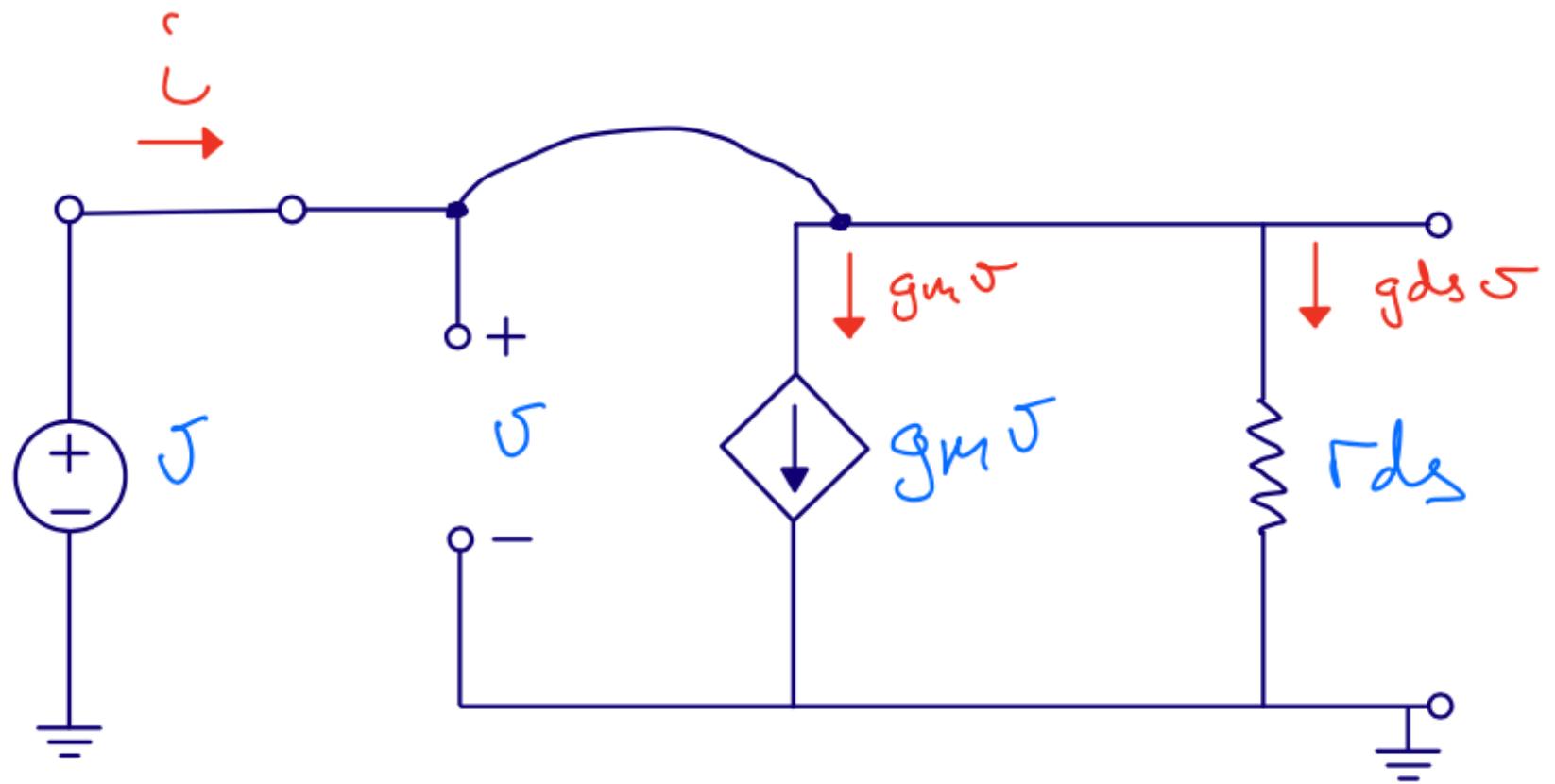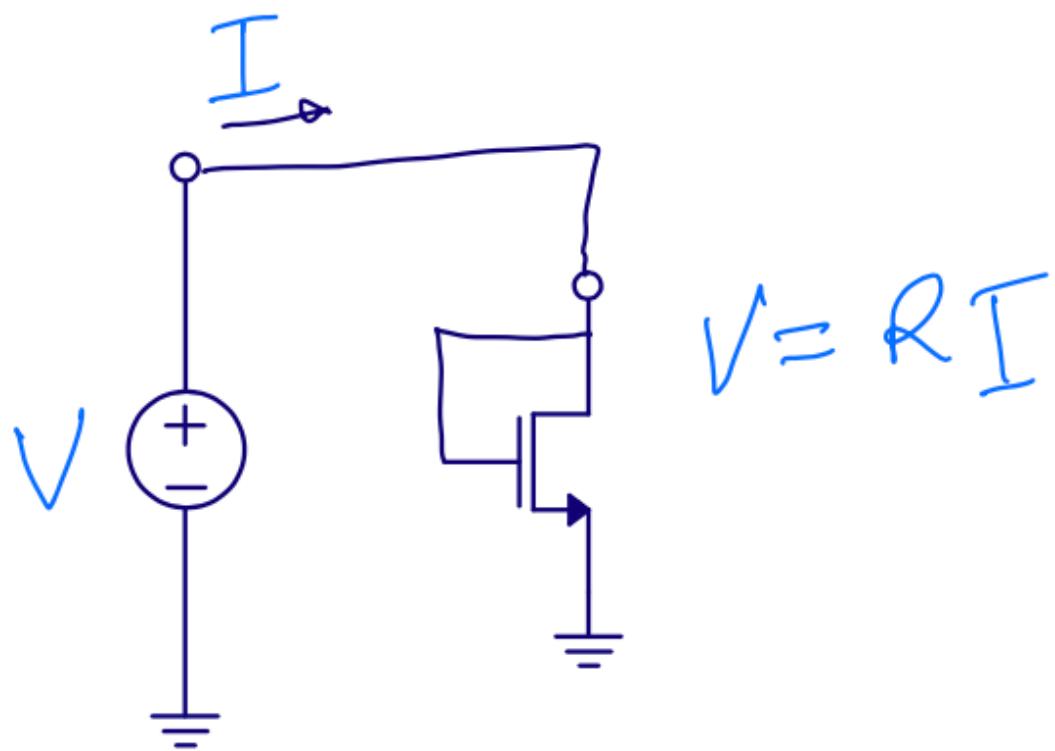

Current mirror r_{in}

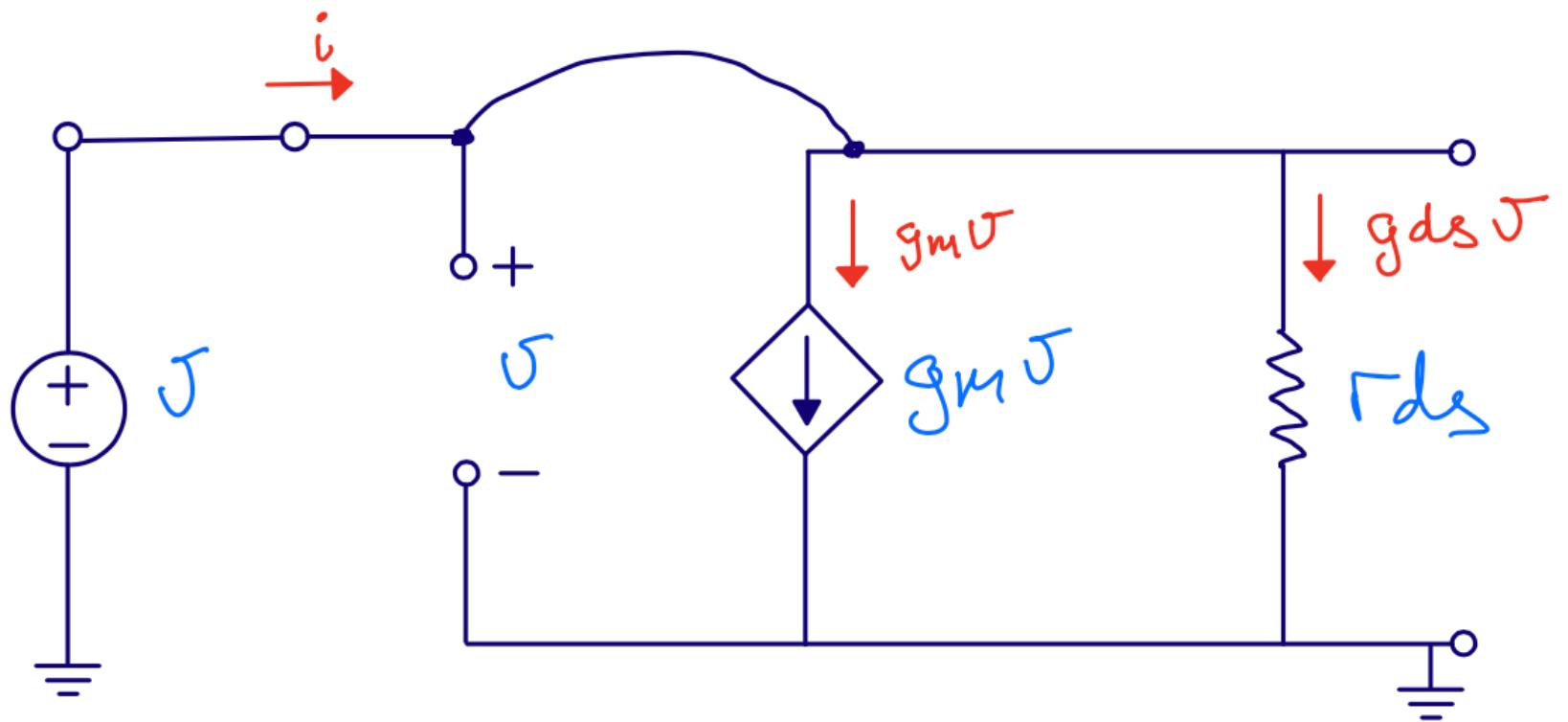

$$r_{ds} = \frac{1}{g_{ds}}$$

$$r_{in} = \frac{v}{i}$$


$$i = g_m v + g_{ds} v$$


$$r_{in} = \frac{1}{g_m + g_{ds}} \approx \frac{1}{g_m}$$

Current mirror r_{out}

Output voltage does not affect v_{gs}

$$r_{out} = r_{ds}$$


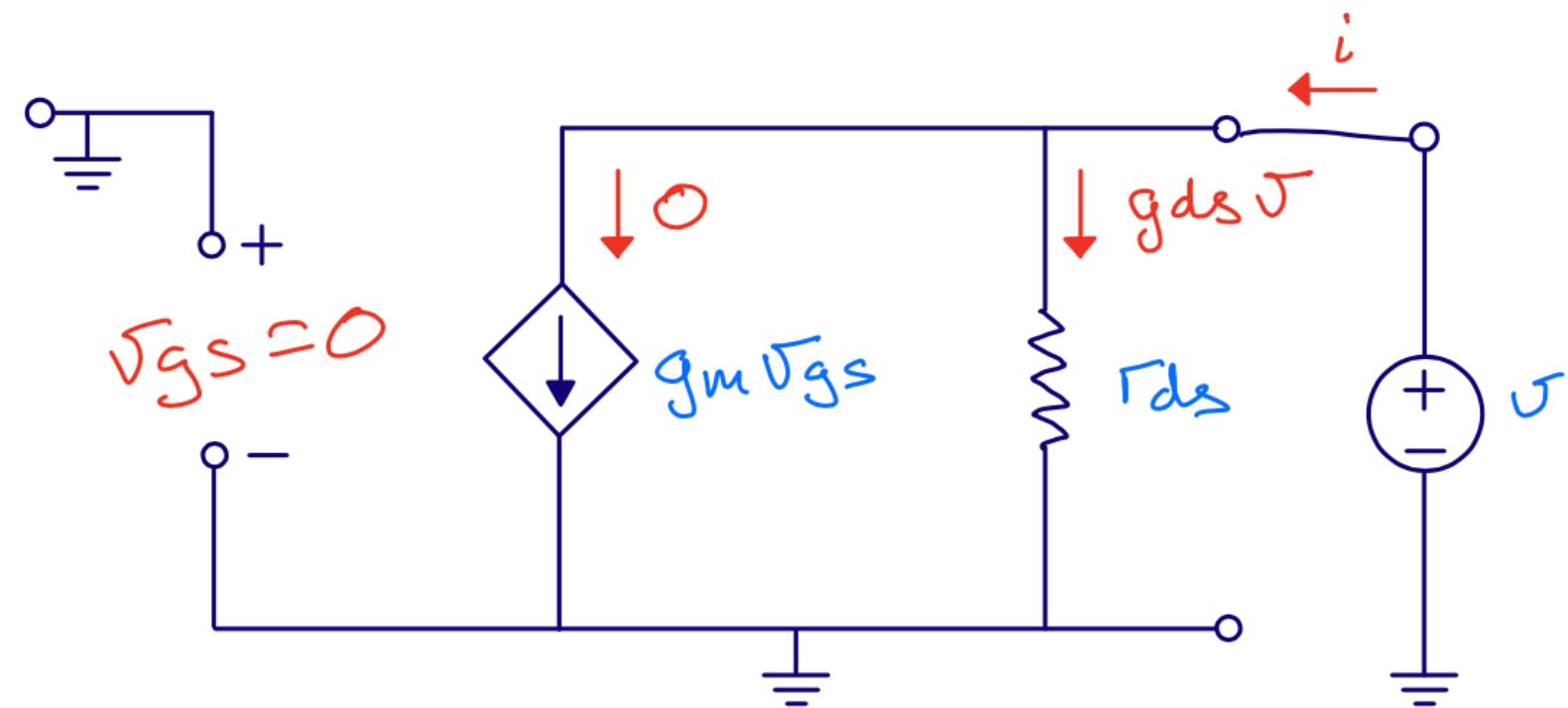



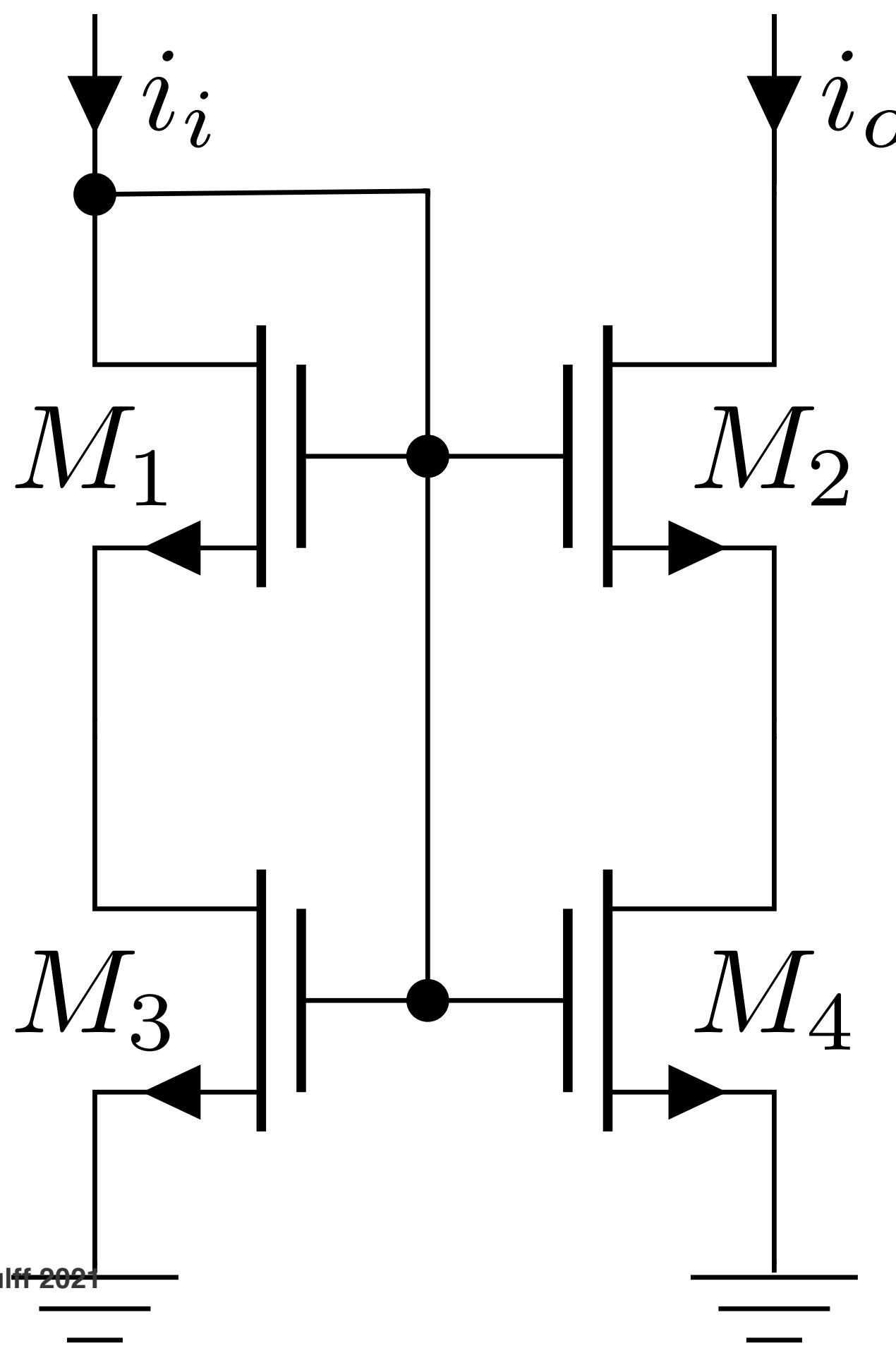




Source degeneration

What is the operating region of M_3 and M_4 ?

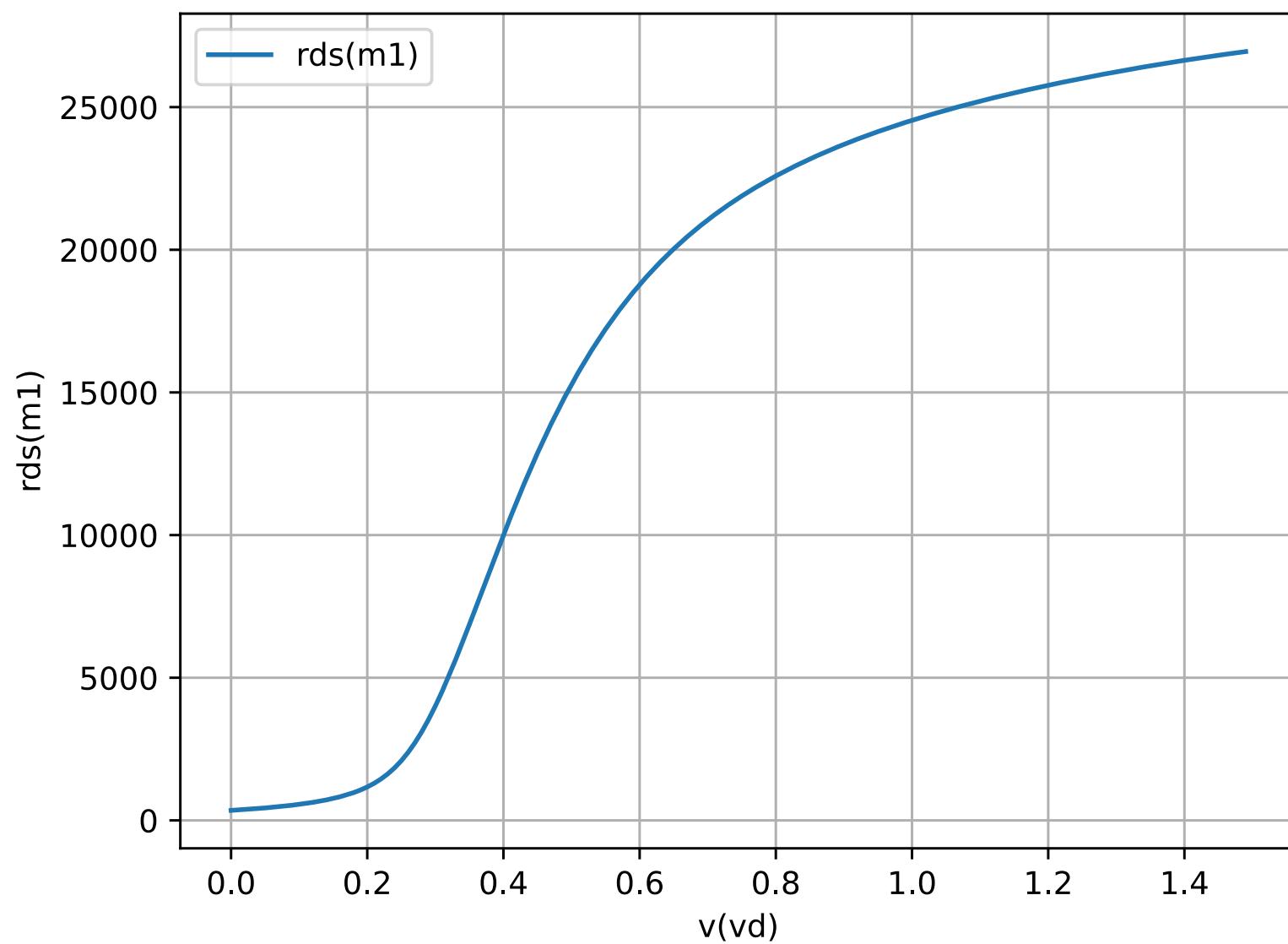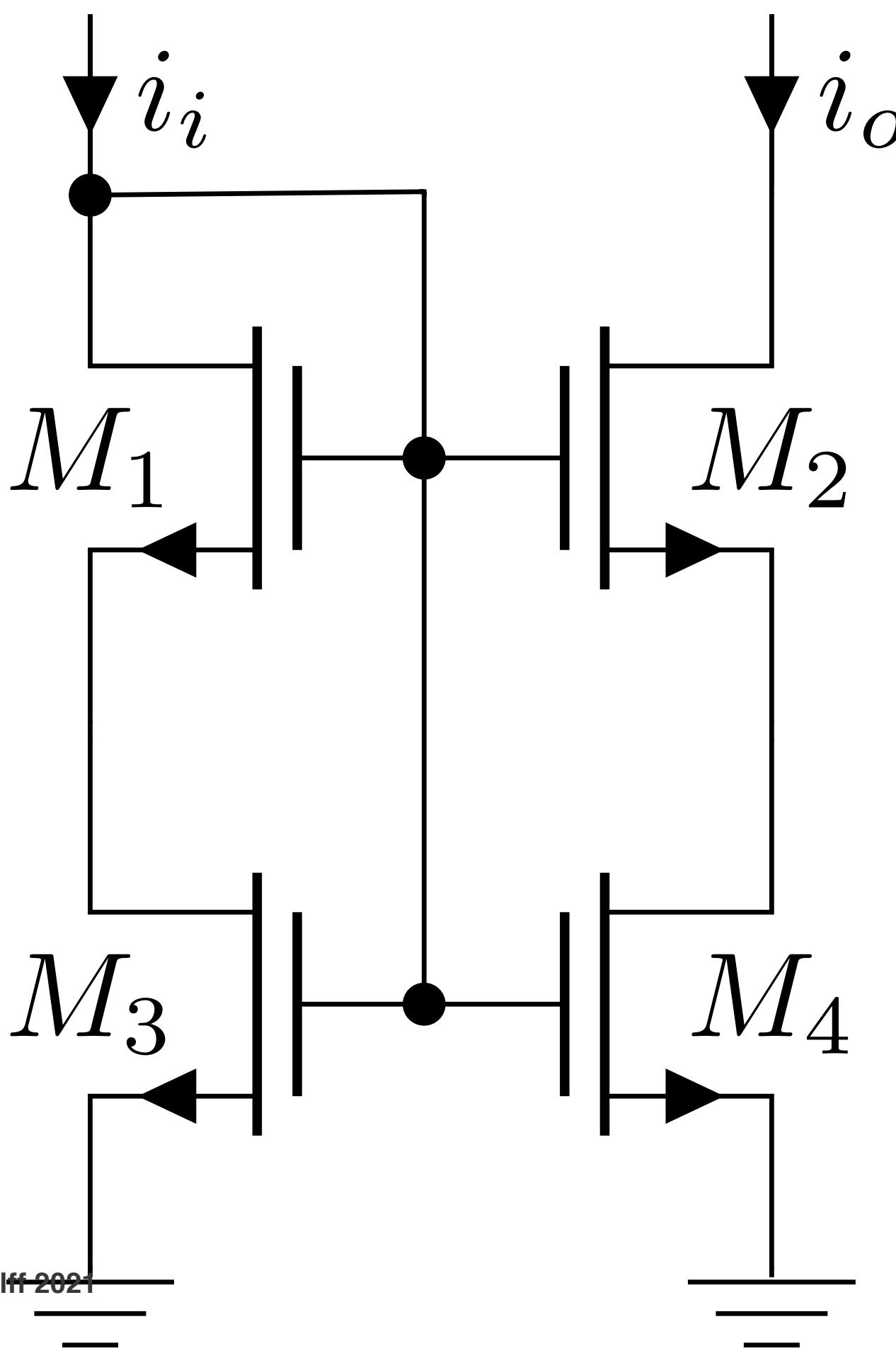What is the operating region of M_1 and M_2 ?



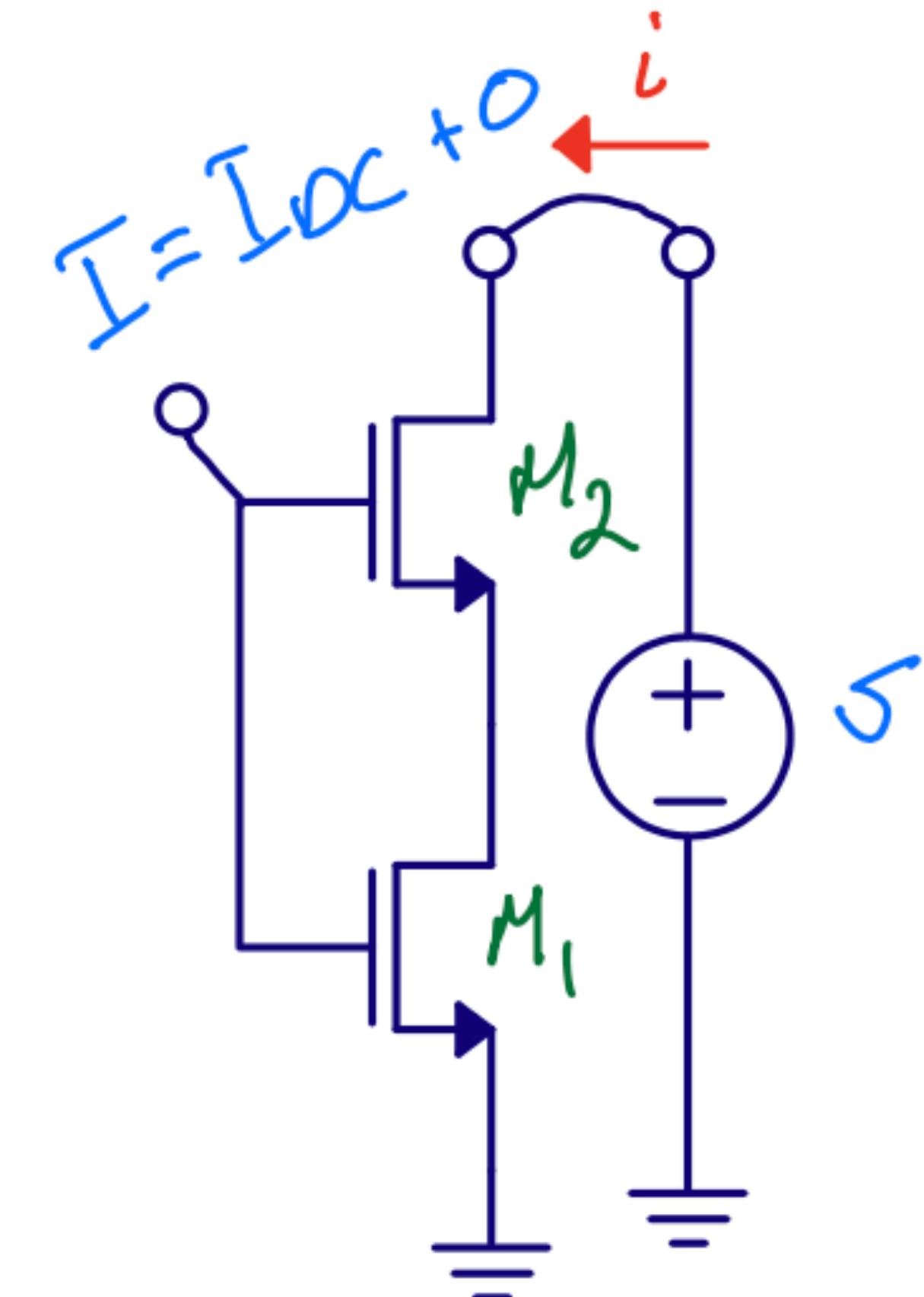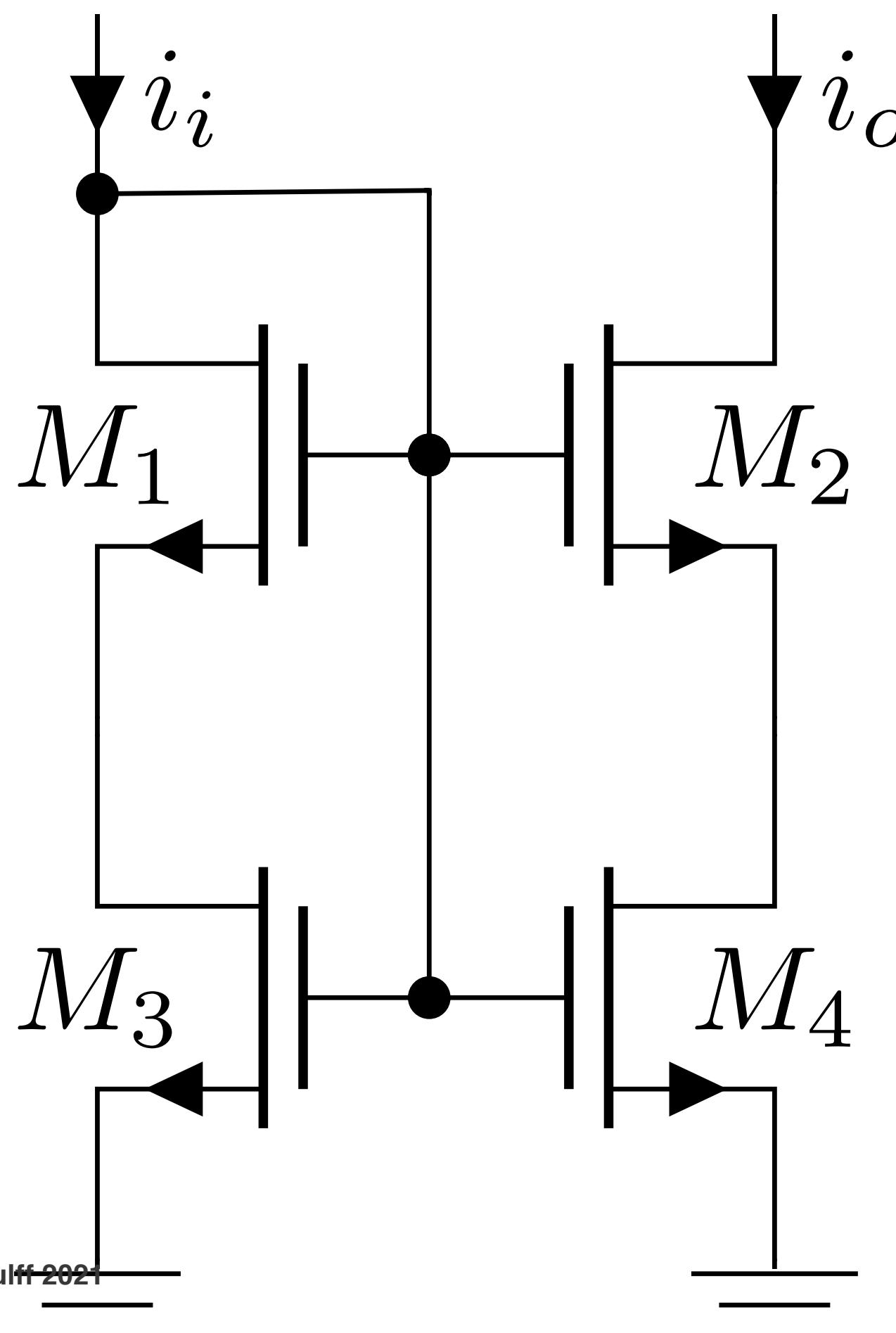

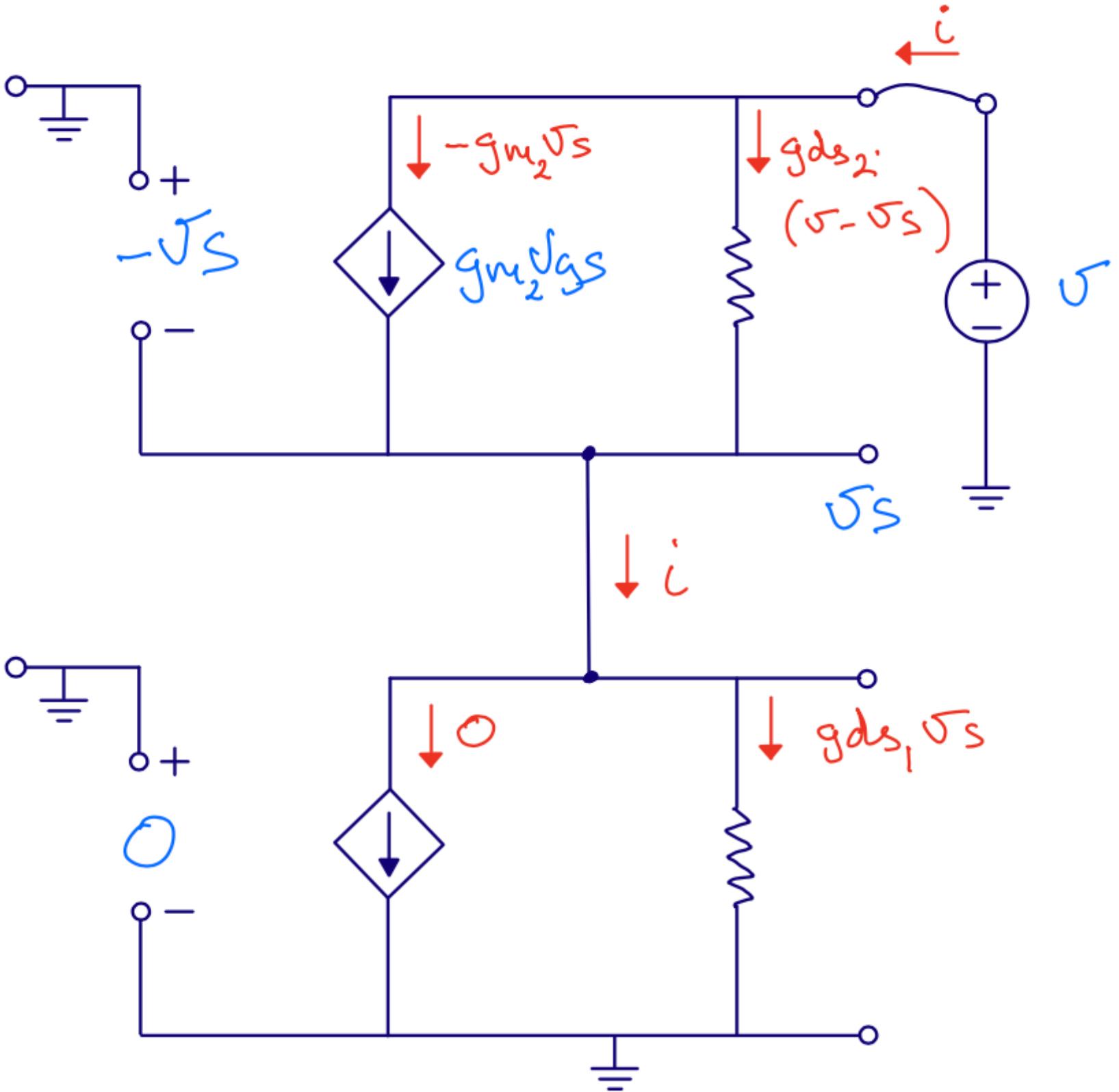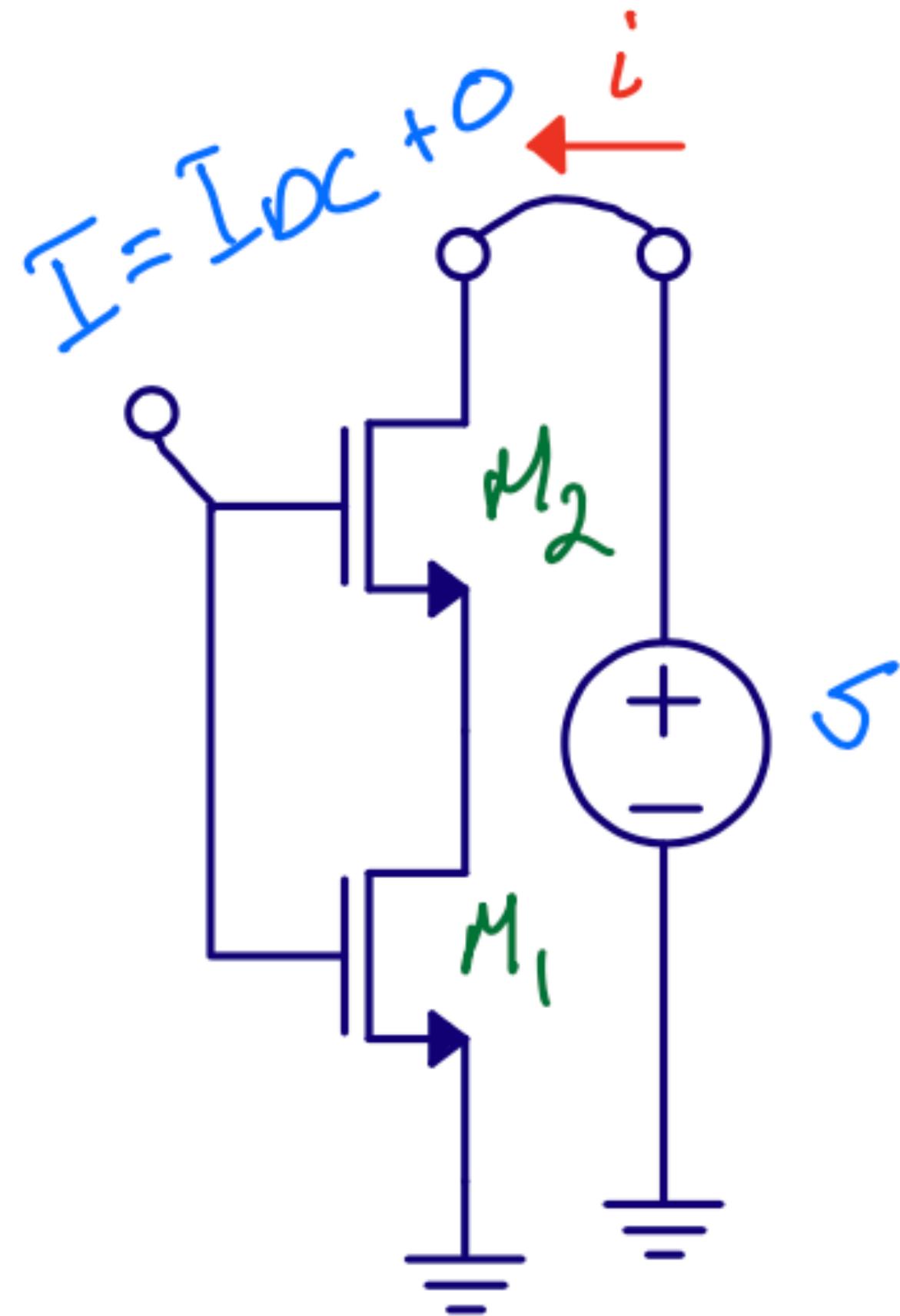

Source degeneration r_{out}



$$v_{gs1} = 0$$

$$v_{gs2} = -v_s$$

$$i = g_{ds1} v_s \Rightarrow v_s = i r_{ds1}$$

$$r_{out} = \frac{v}{i}$$
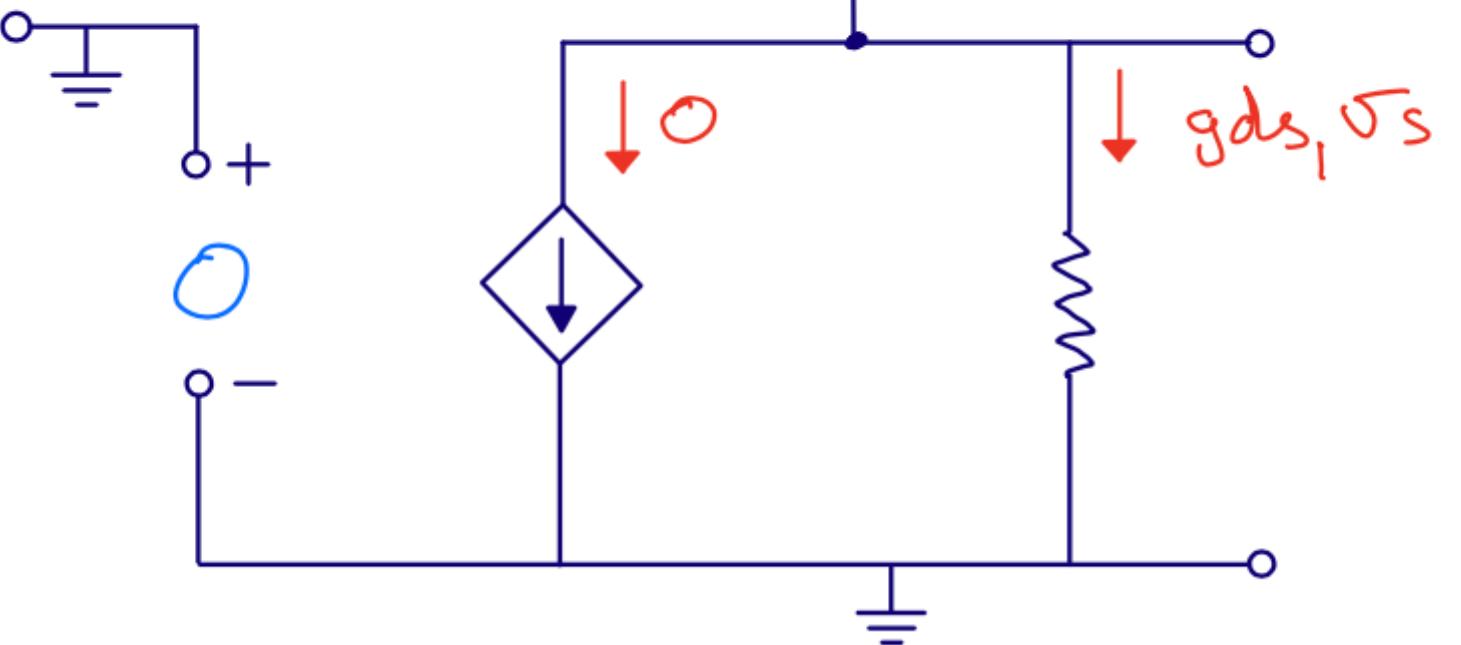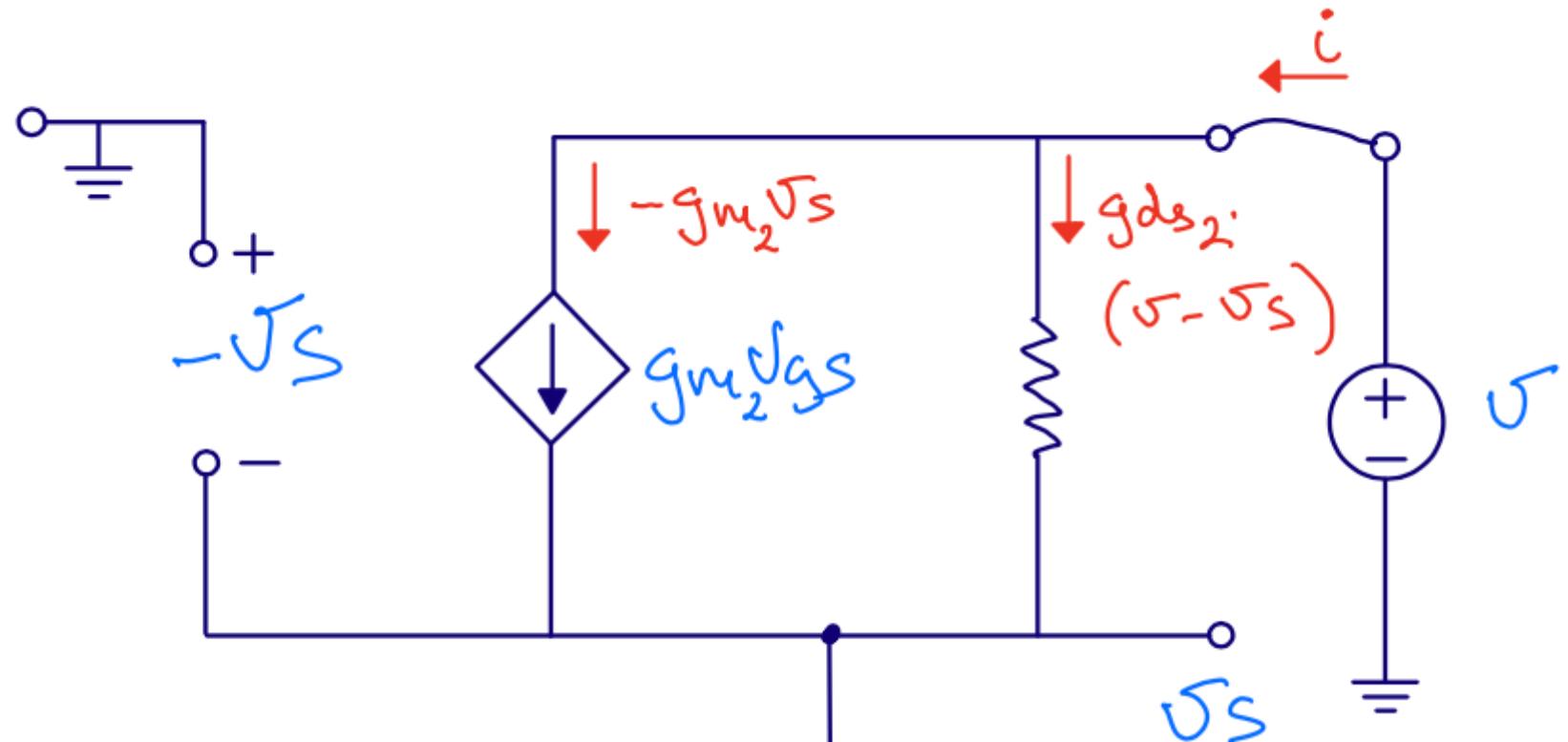
$$i = -g_{m2} v_s + \frac{v - v_s}{r_{ds2}}$$



$$i = -g_{m2}v_s + \frac{v - v_s}{r_{ds2}} \text{ insert } v_s = ir_{ds1}$$



$$i = -ig_{m2}r_{ds1} + \frac{v - ir_{ds1}}{r_{ds2}}$$


$$ir_{ds2} + ig_{m2}r_{ds1}r_{ds2} + ir_{ds1} = v$$

$$r_{ds2} + g_{m2}r_{ds1}r_{ds2} + r_{ds1} = \frac{v}{i}$$


$$r_{out} = r_{ds2} \left[1 + r_{ds1} \left(\frac{1}{r_{ds2}} + g_{m2} \right) \right]$$
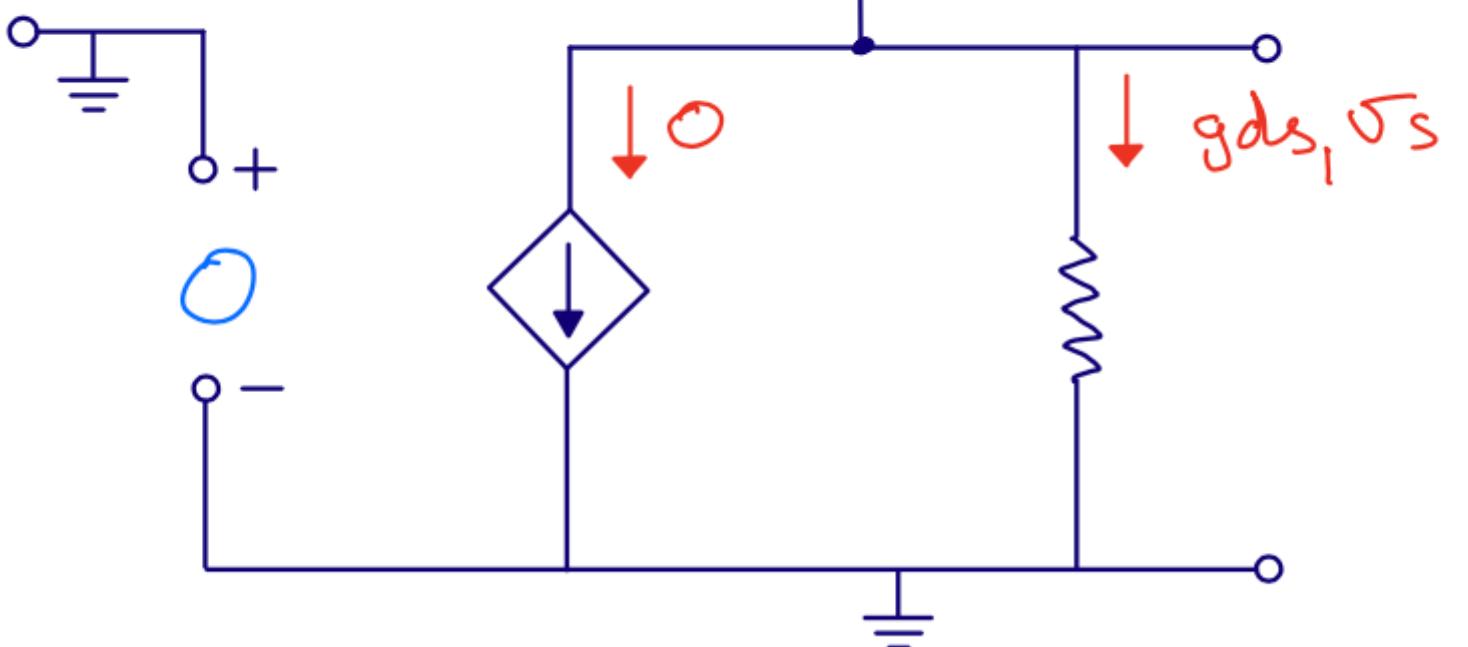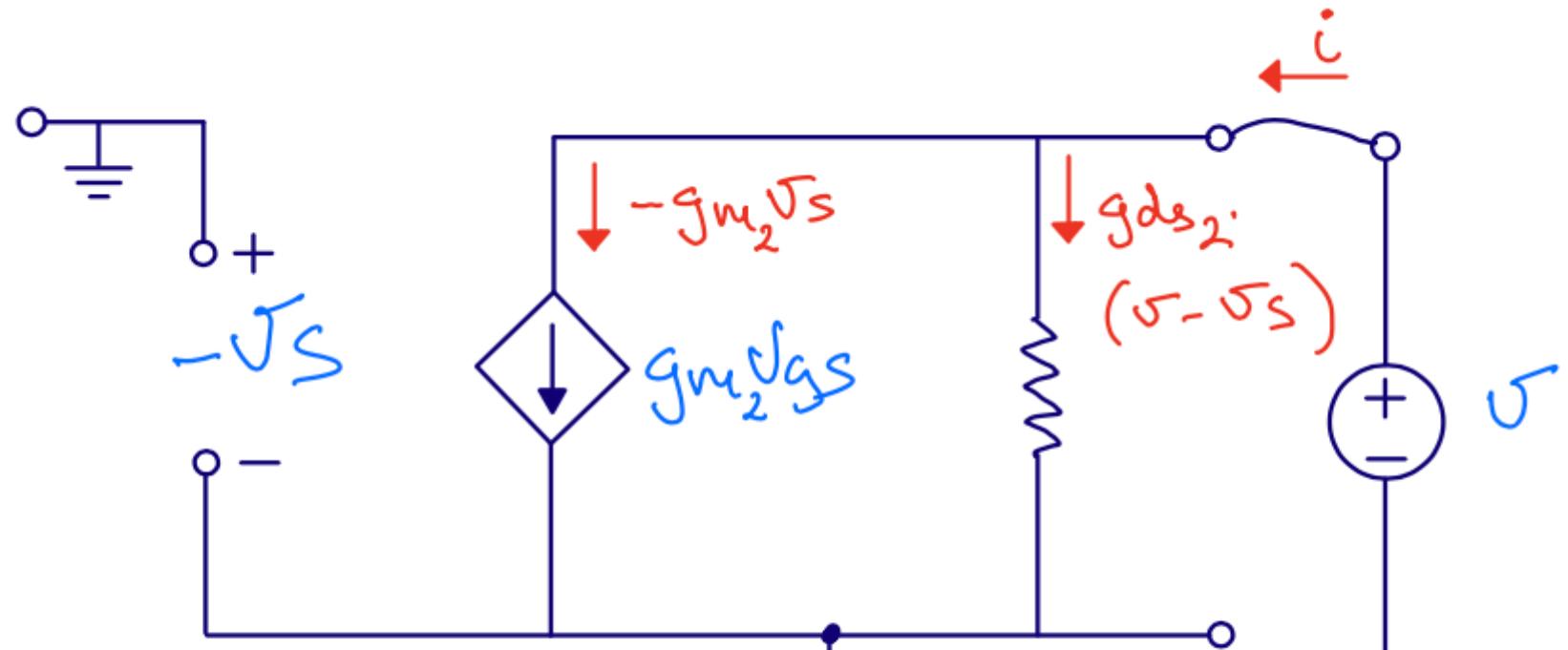
$$r_{out} = r_{ds2} [1 + r_{ds1}(g_{m2} + g_{ds2})]$$



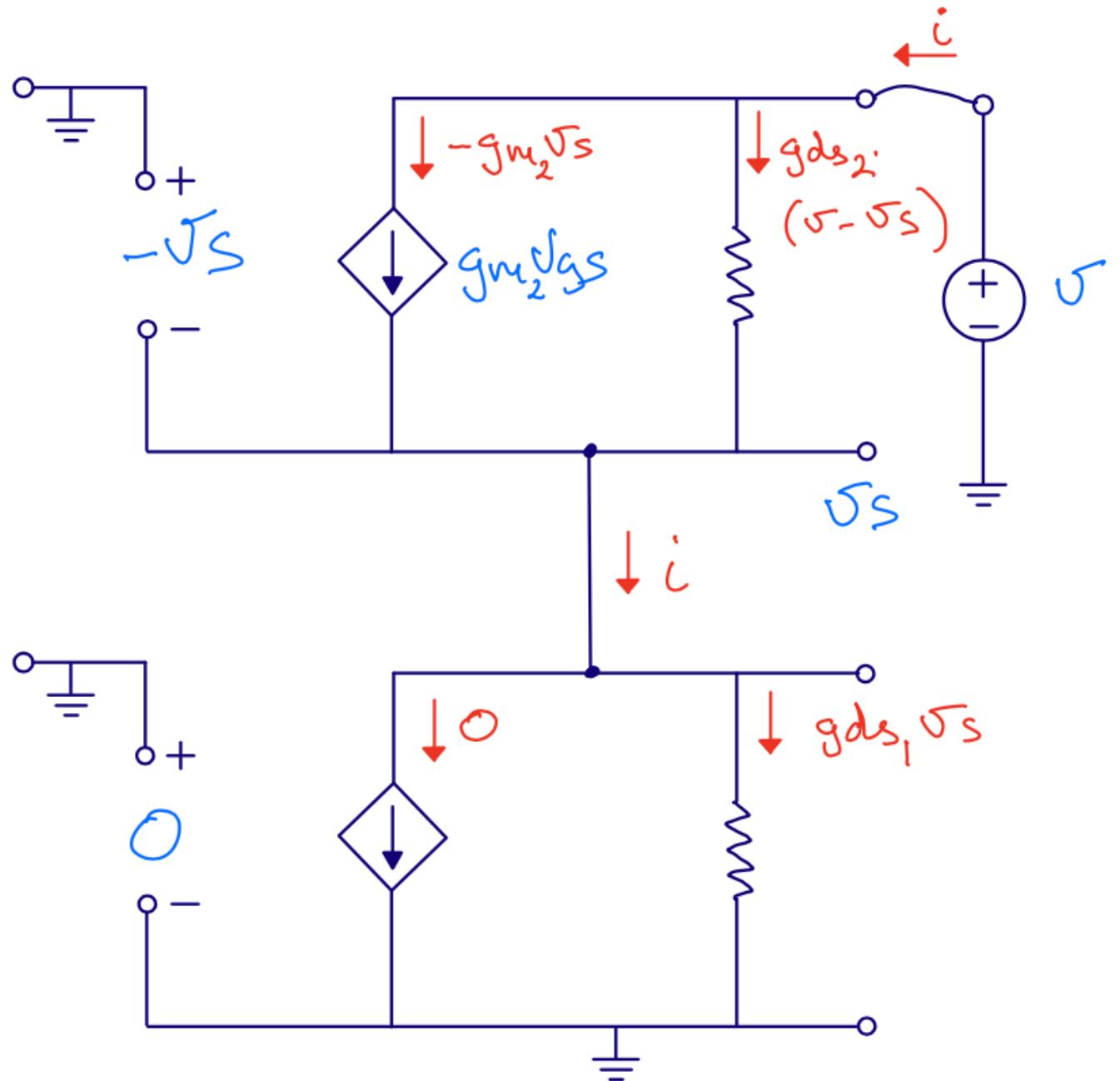
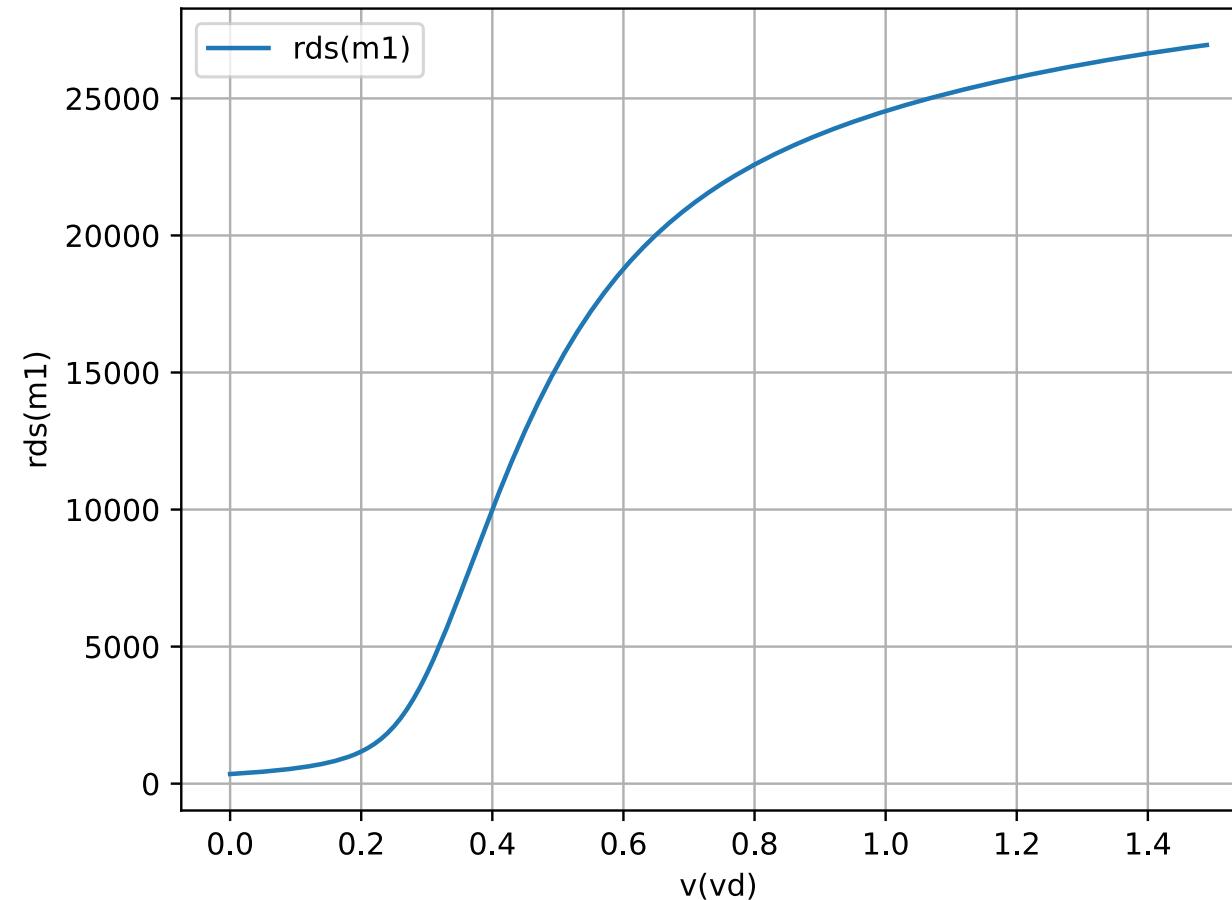
$$r_{out} = r_{ds2}[1 + r_{ds1}(g_{m2} + g_{ds1})]$$





Cascode current mirror

Same equation as source degeneration,
but M_2 is in saturation


$$r_{ds2(\text{saturation})} > r_{ds2(\text{linear})}$$
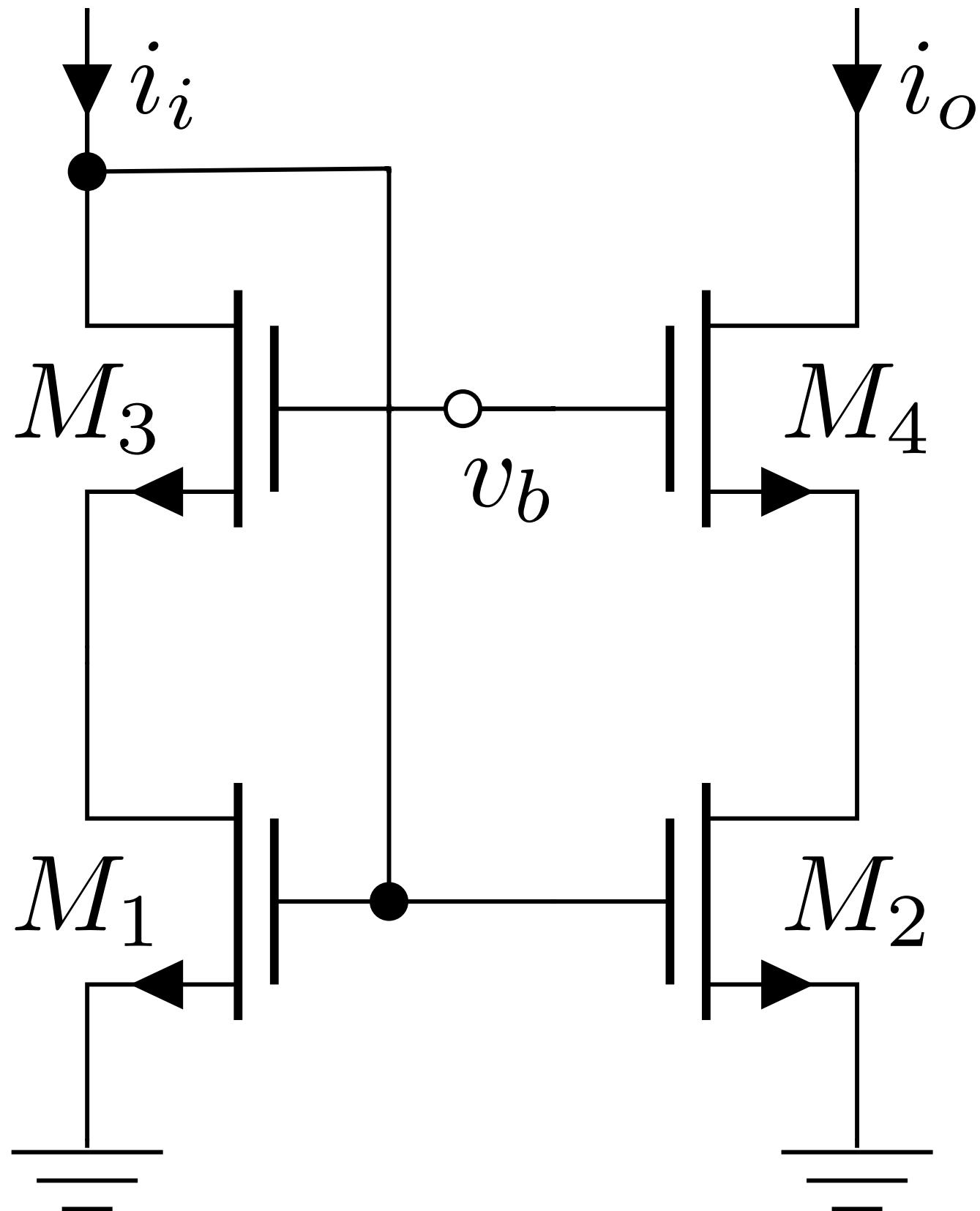
$$r_{out} = r_{ds4} [1 + r_{ds2} (g_{m4} + g_{ds2})]$$




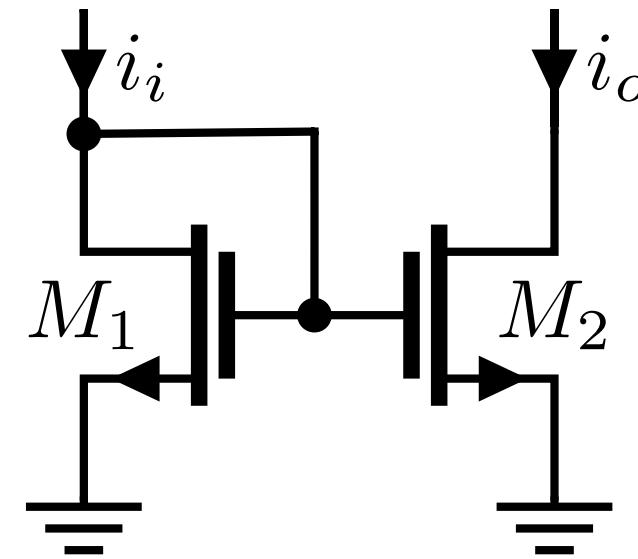


a) "normal"

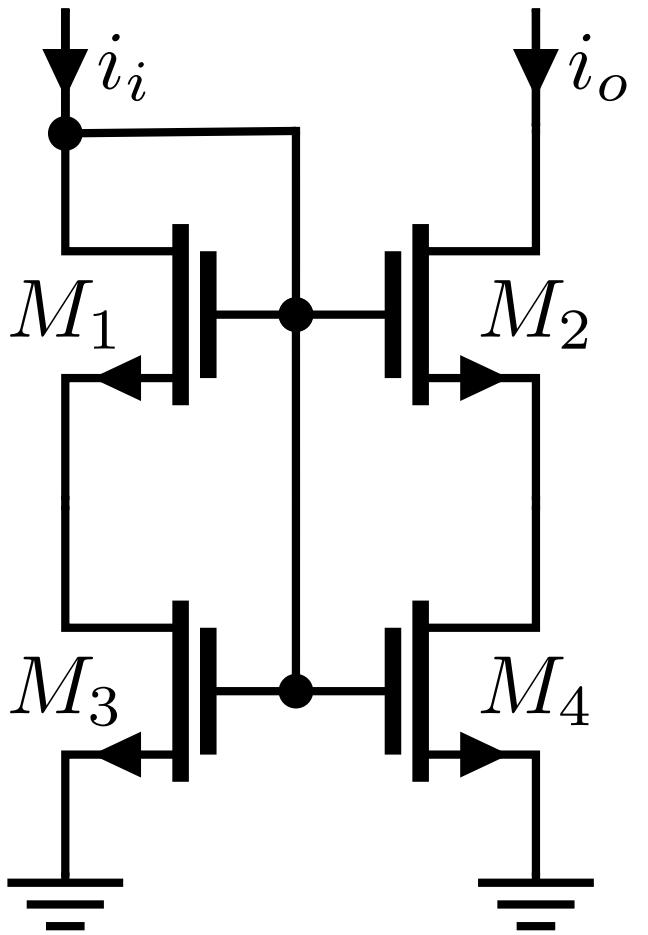

b) Self Cascode

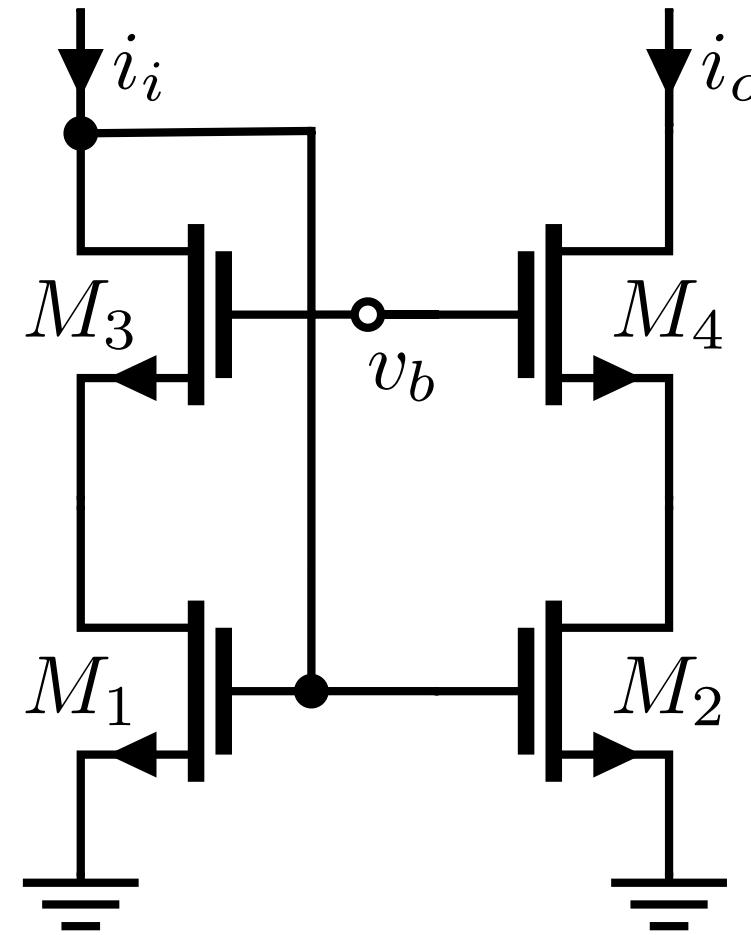

c) Cascode

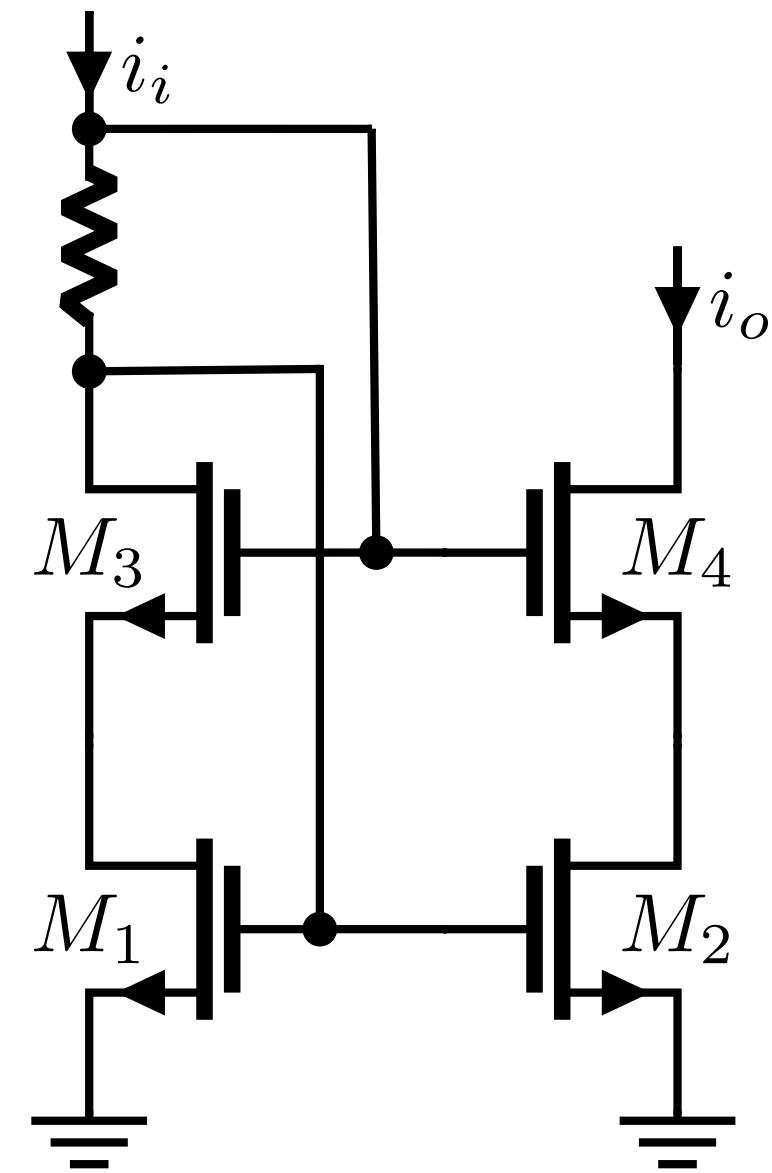

d) Lazy Cascode

One more current mirror ...

"High speed, high gain OTA in a digital 90nm CMOS technology" Berntsen, Wulff, Ytterdal

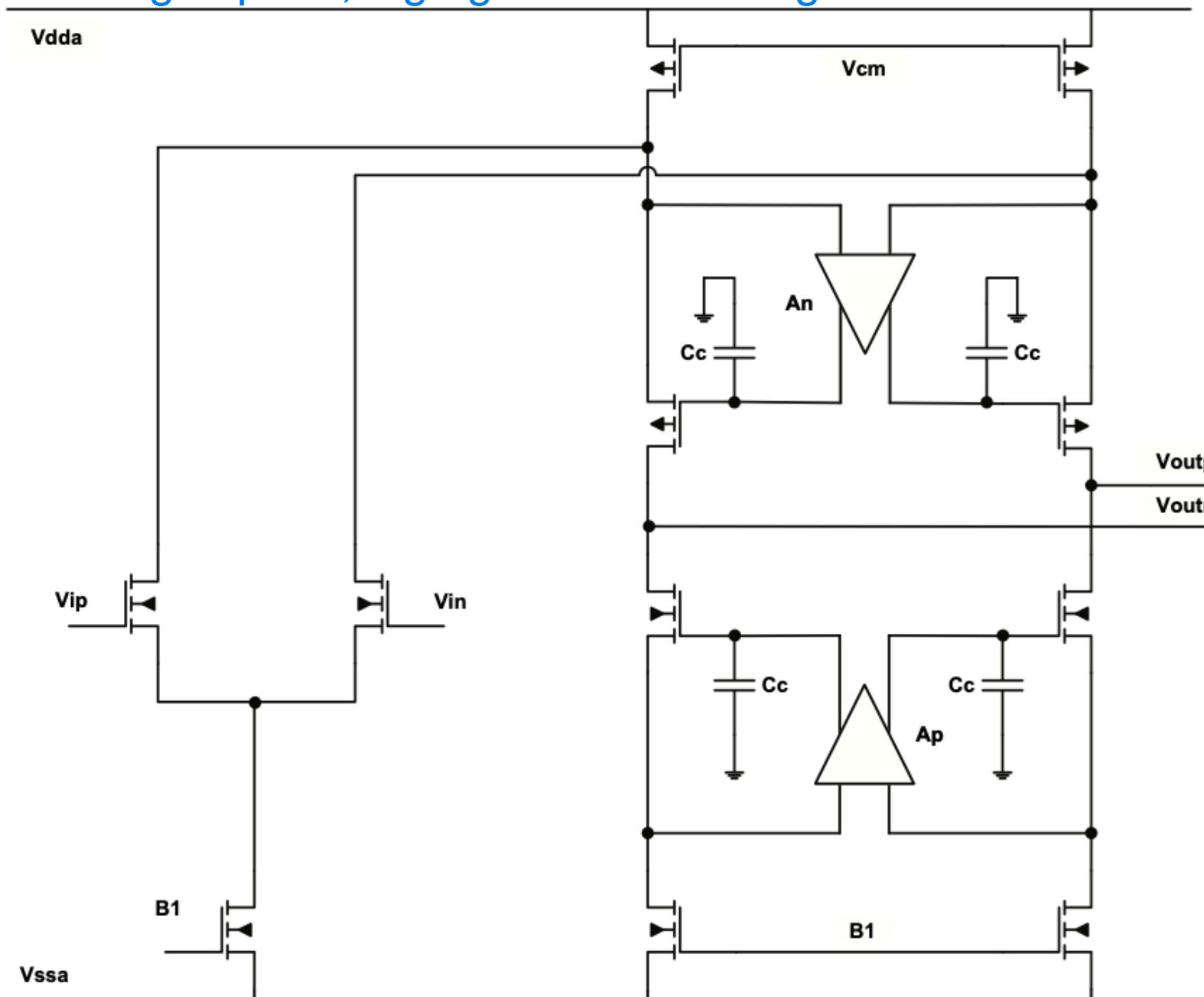


Fig. 2. OTA circuit with fully differential gain enhancement.


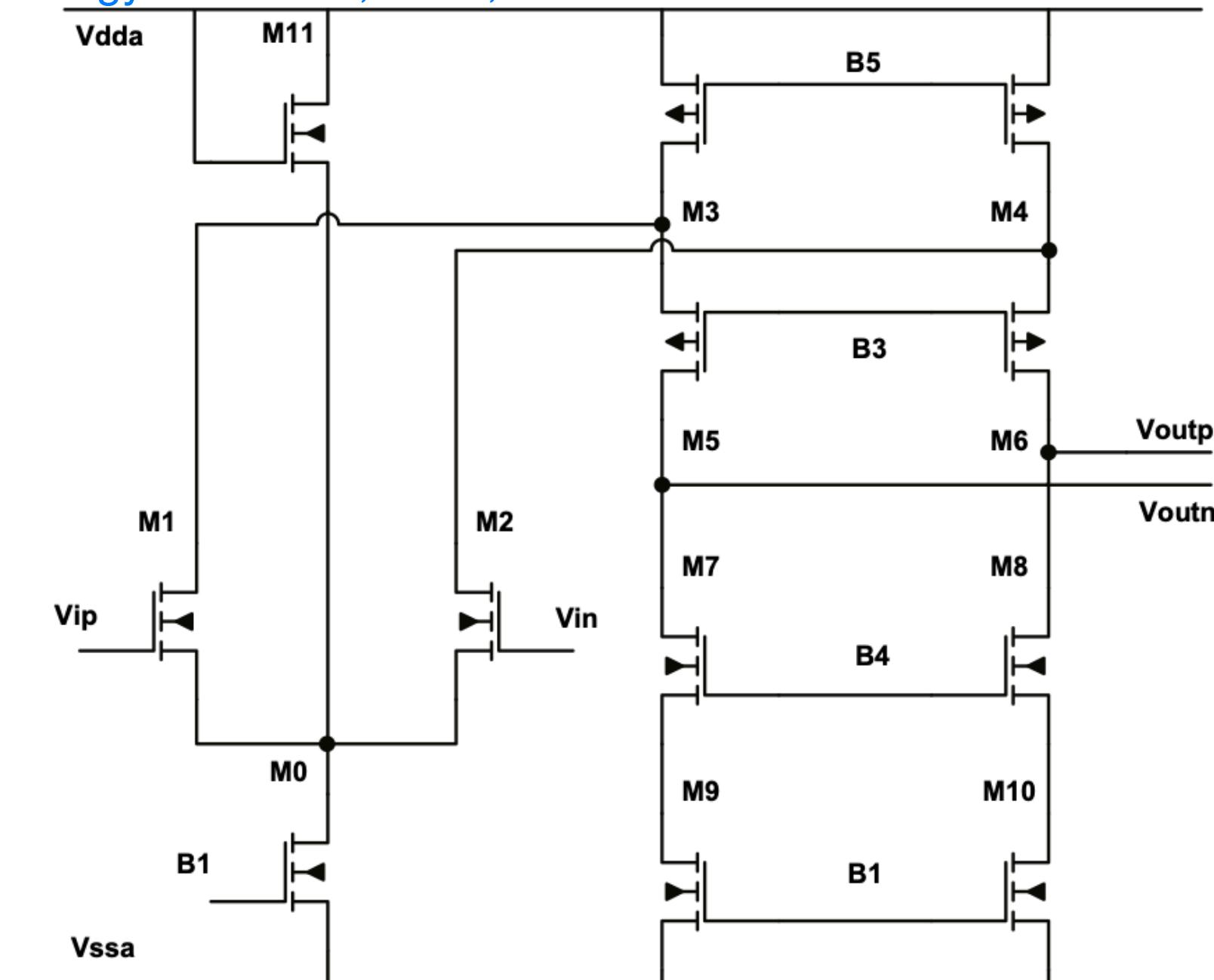


Fig. 3. Fully differential supplemental OTA .

Amplifiers

Source follower



Source follower

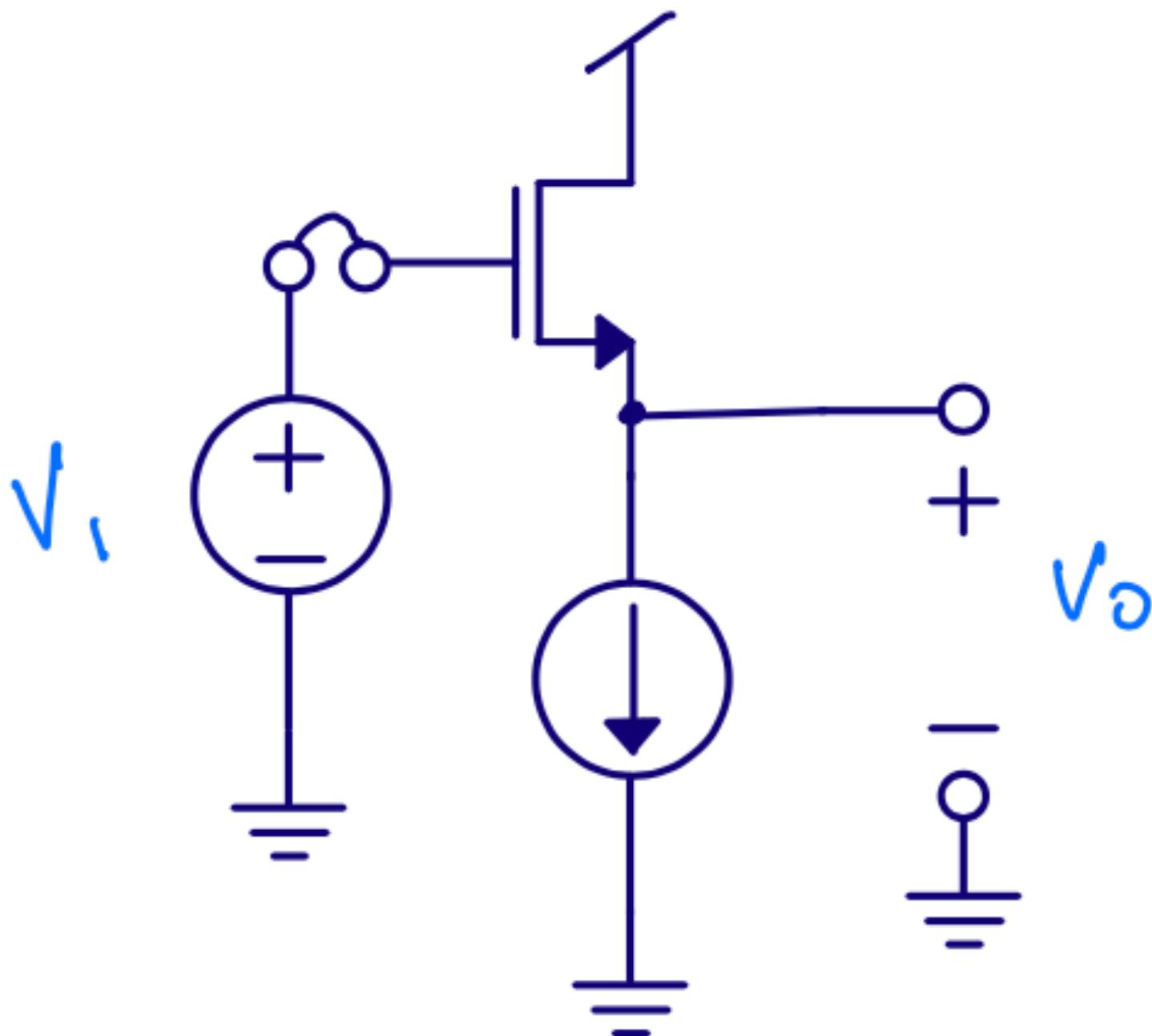

Input resistance $\approx \infty$

$$\text{Gain } A = \frac{v_o}{v_i} ?$$

Output resistance r_{out} ?

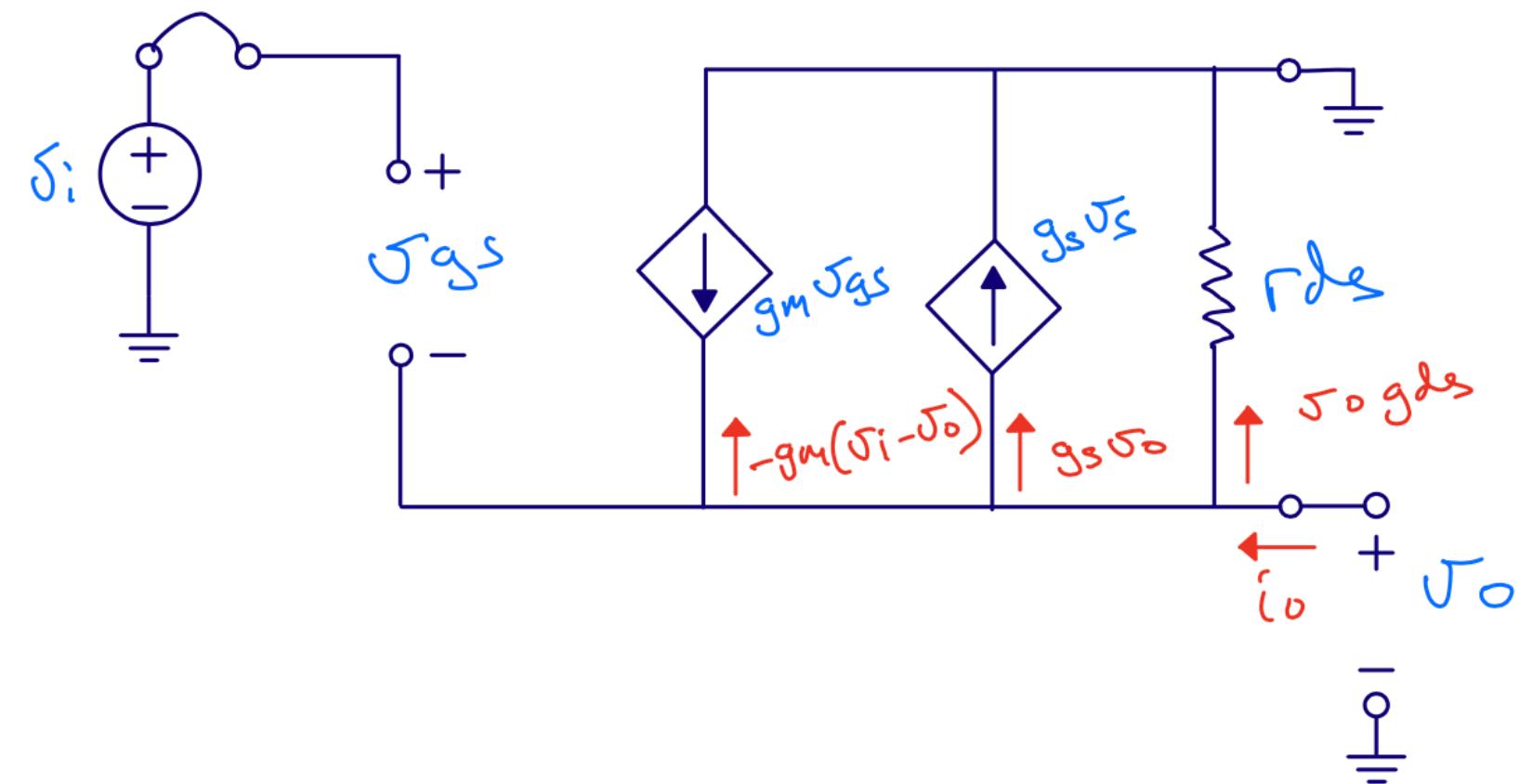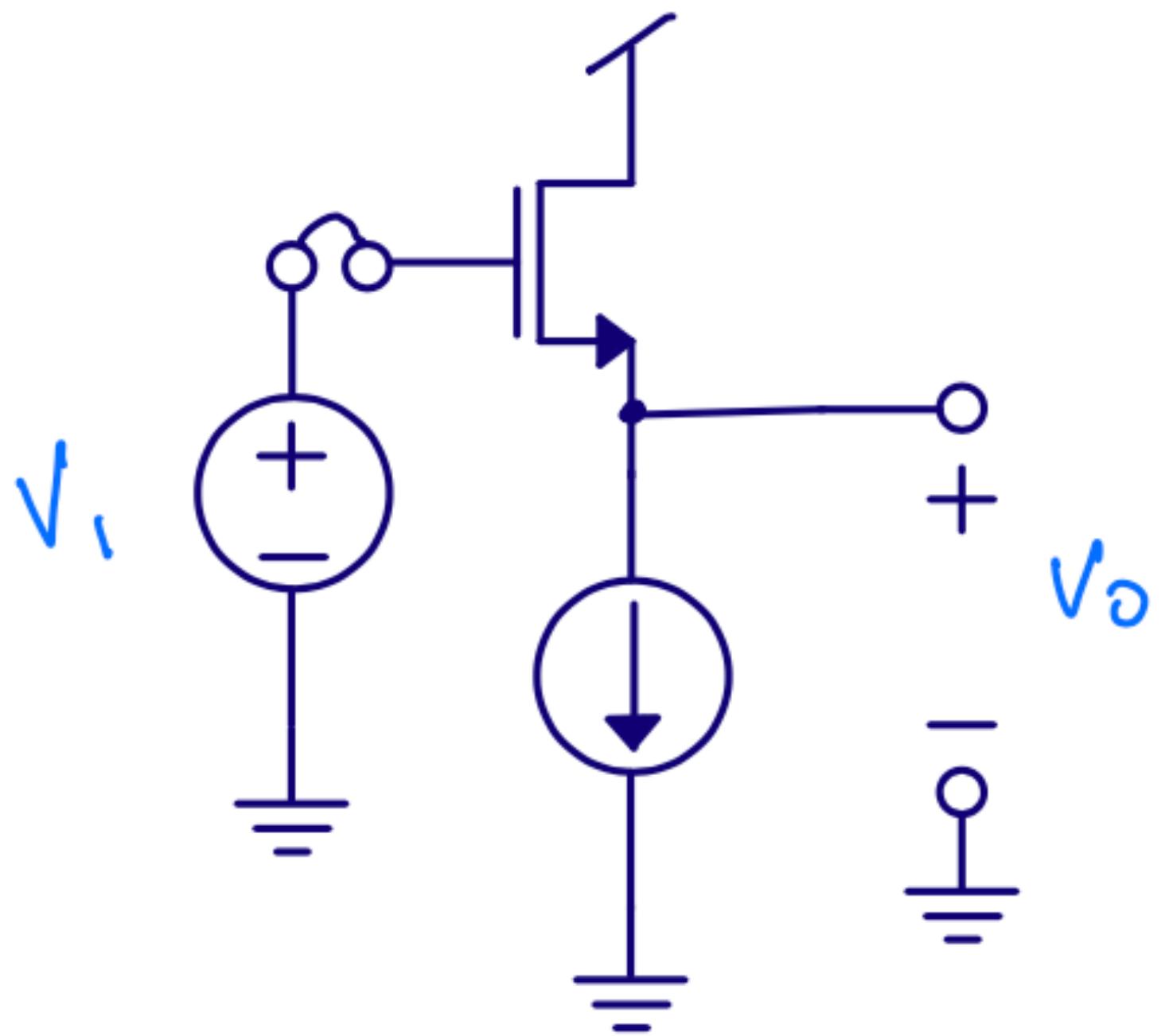


Source follower - Gain

$$i_o = v_o(g_{ds} + g_s) - g_m v_i + v_o g_m$$

$$i_o = 0$$

$$g_m v_i = v_o(g_m + g_s + g_{ds})$$
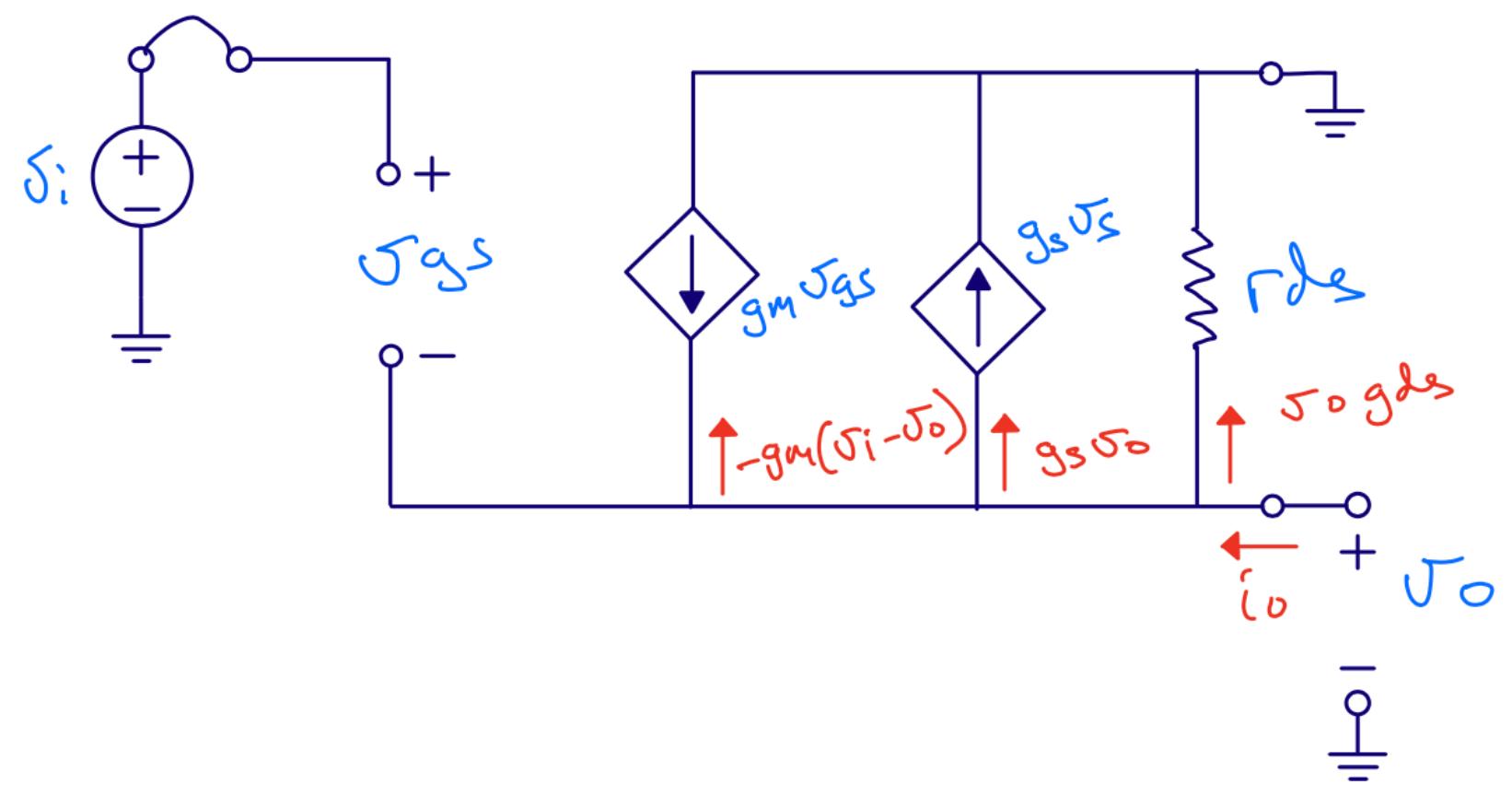
$$A = \frac{v_o}{v_i} = \frac{g_m}{g_m + g_{ds} + g_s}$$



Gain is less than 1

Source follower - r_{out}


$$i_o = v_o(g_{ds} + g_s) - g_m v_i + v_o g_m$$



$$v_i = 0$$

$$i_o = v_o(g_{ds} + g_s + g_m)$$

$$r_{out} = \frac{v_o}{i_o} = \frac{1}{g_m + g_{ds} + g_s}$$

$$r_{out} \approx \frac{1}{g_m}$$


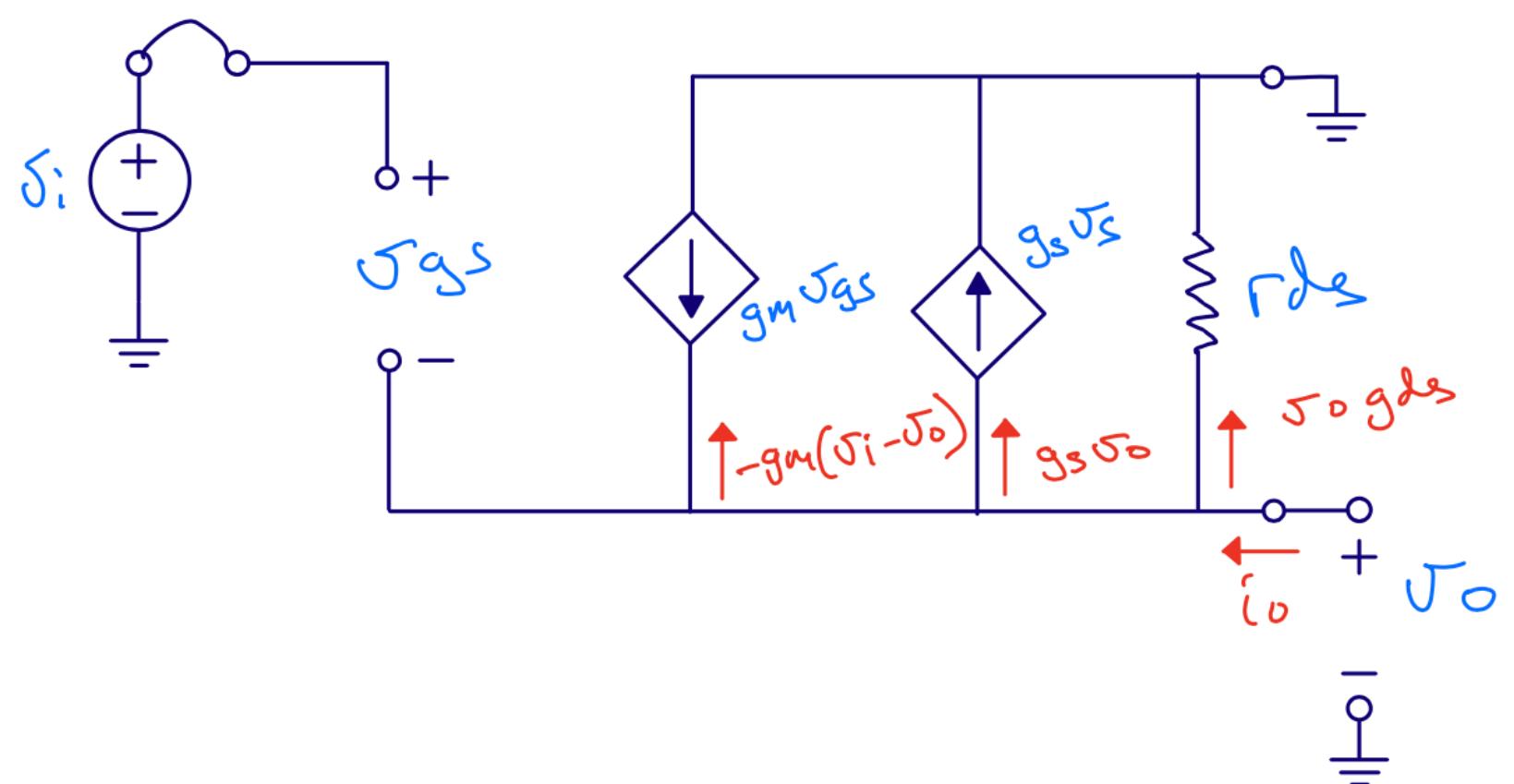


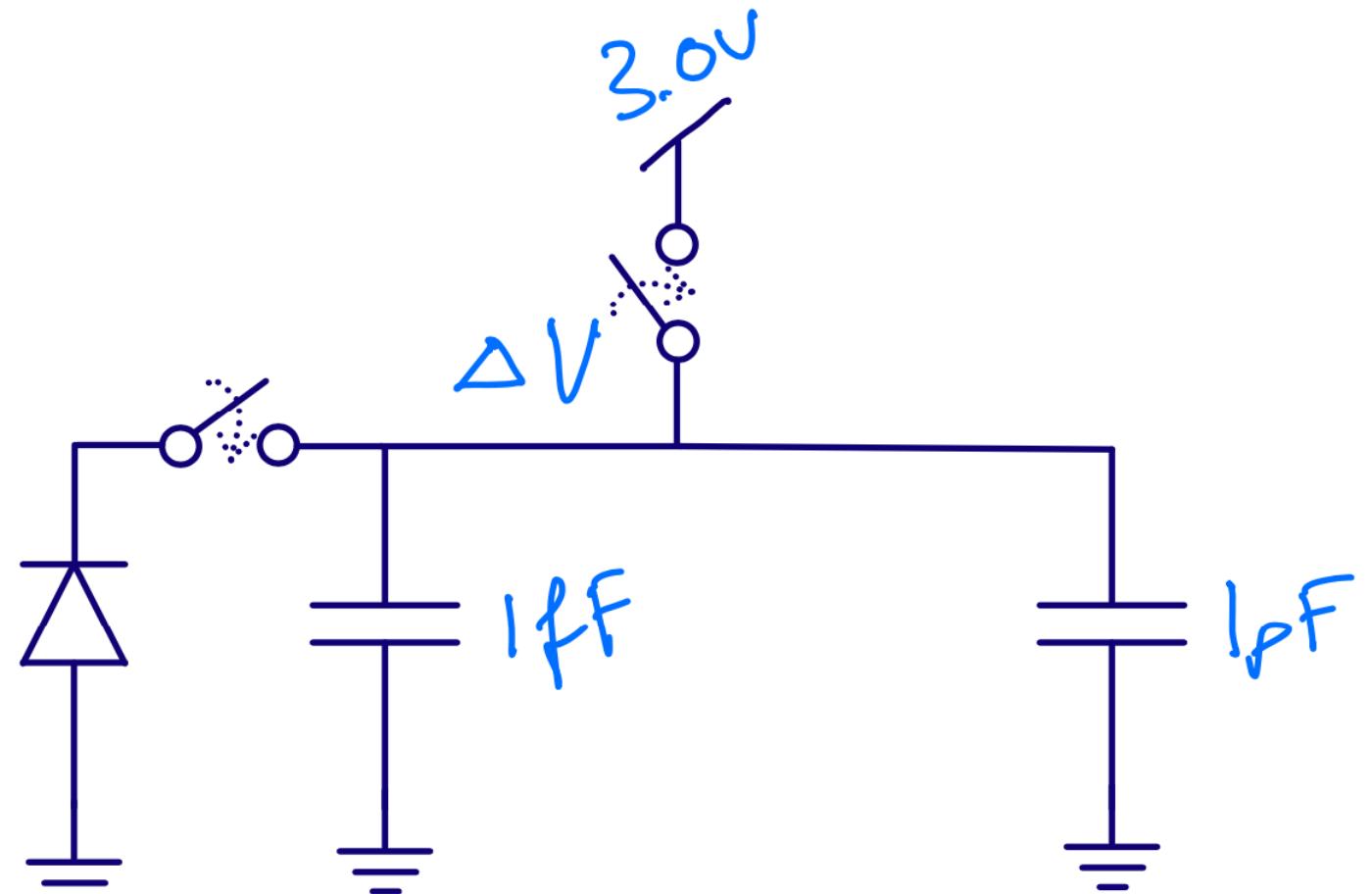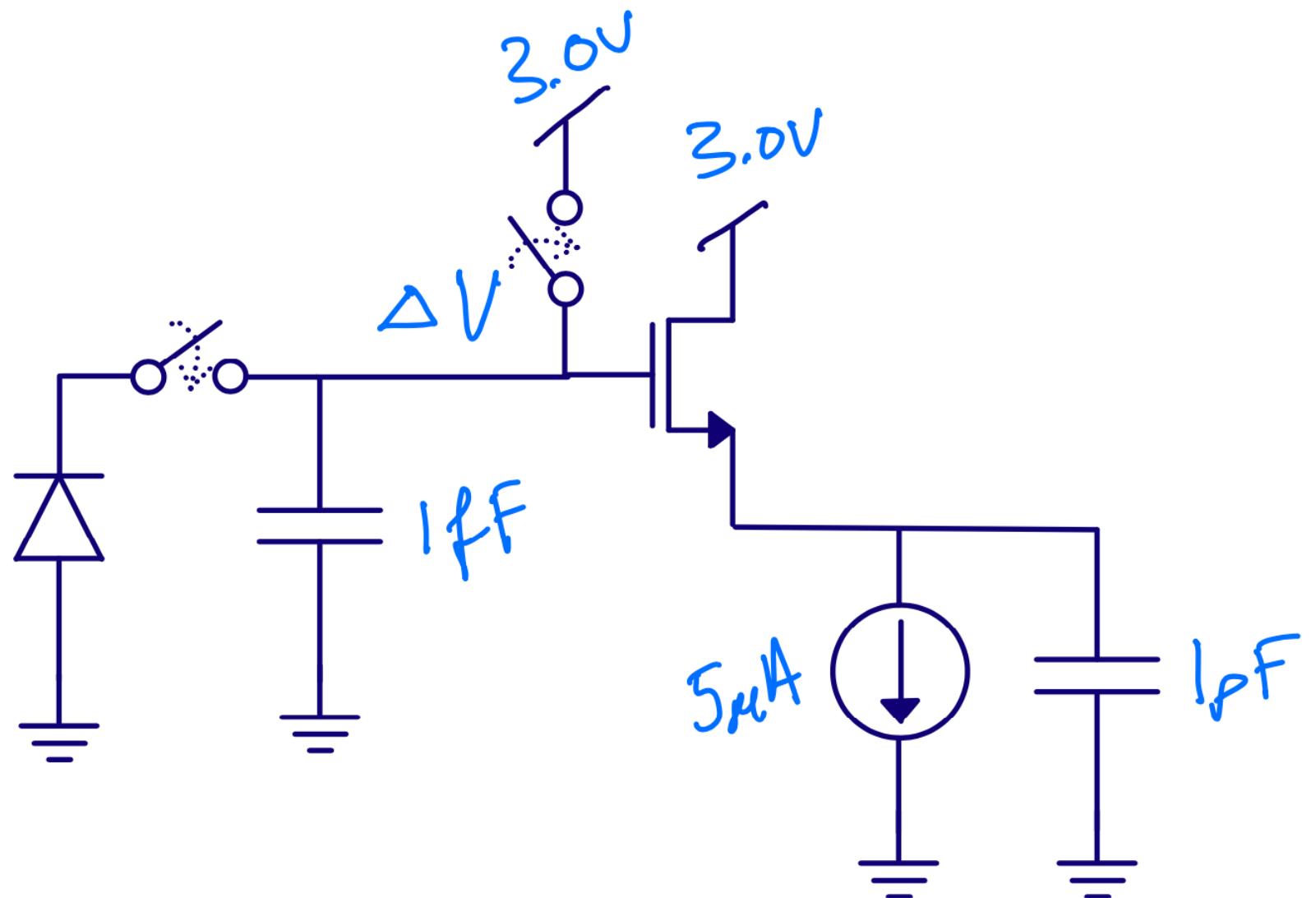

Assume 100 electrons


$$\Delta V = Q/C = -1.6 \times 10^{-19} \times 100/(1 \times 10^{-15}) = -16 \text{ mV}$$
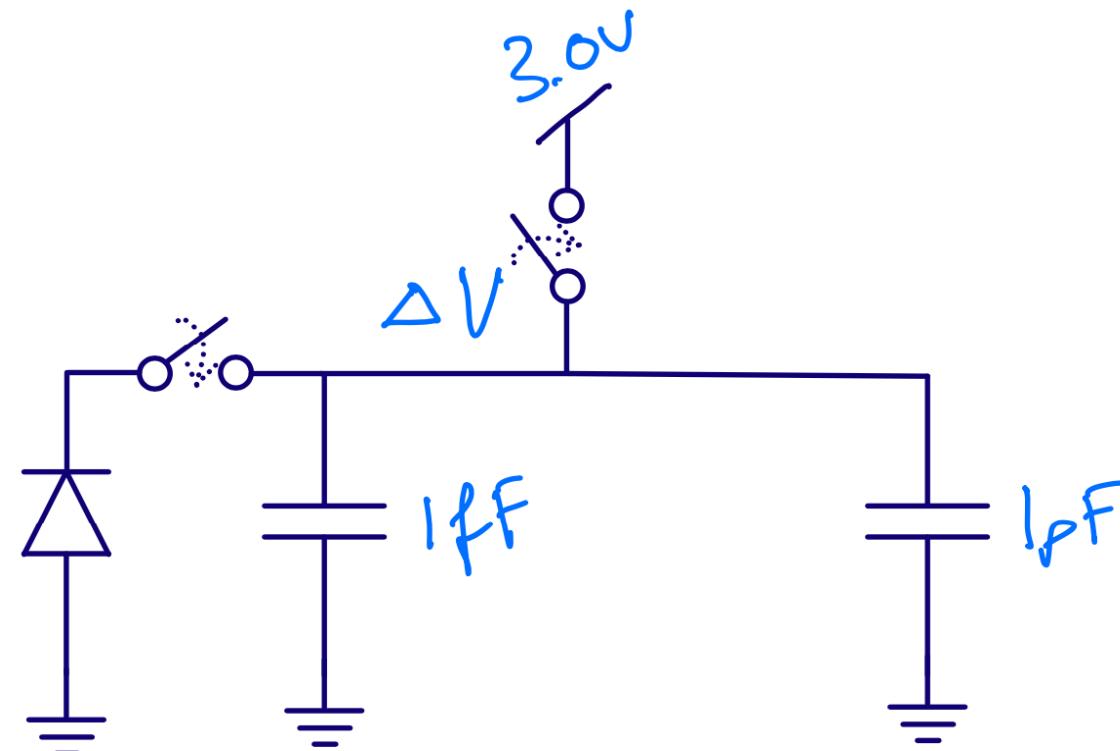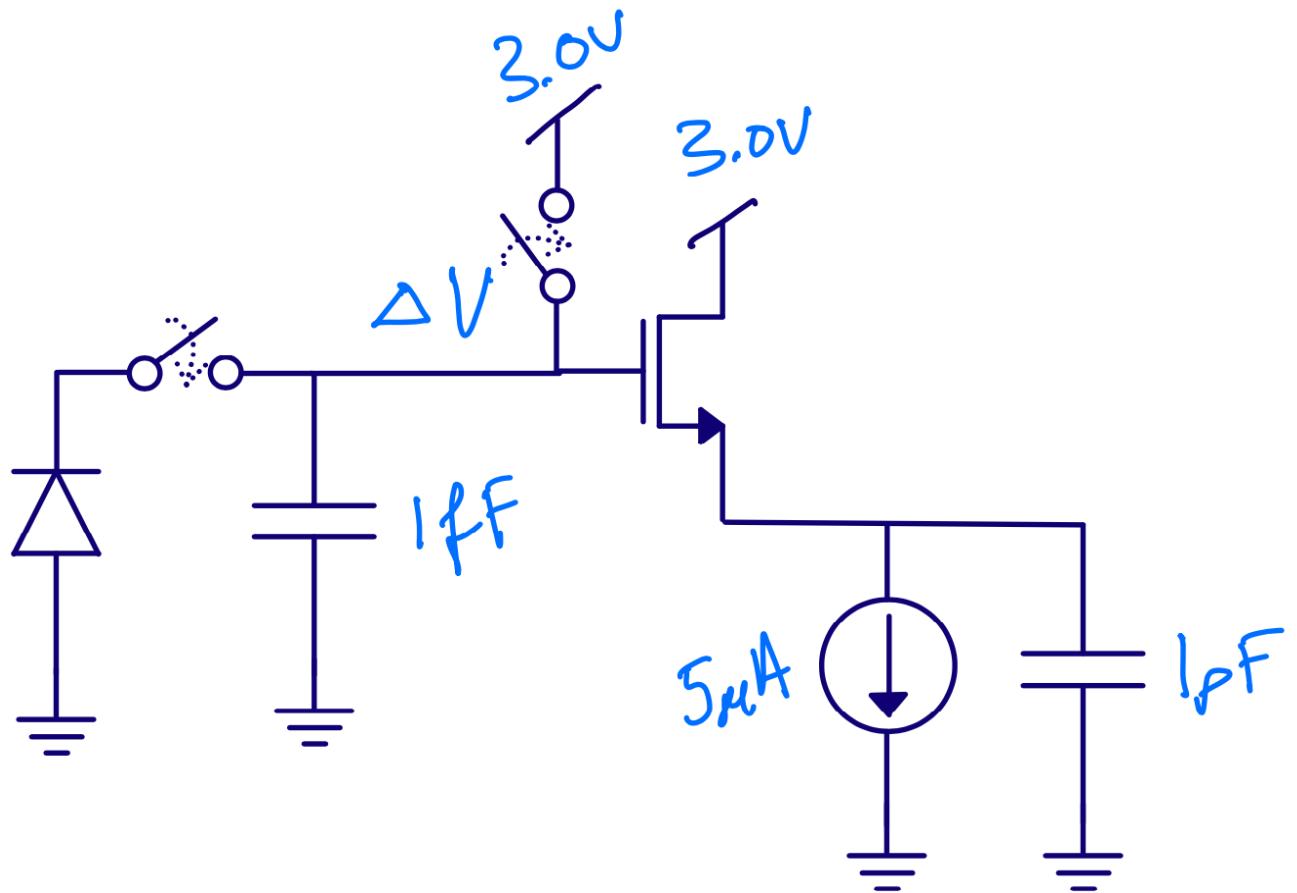
$$\Delta V = Q/C = -1.6 \times 10^{-19} \times 100/(1 \times 10^{-12}) = -16 \text{ uV}$$



Common gate



Common gate

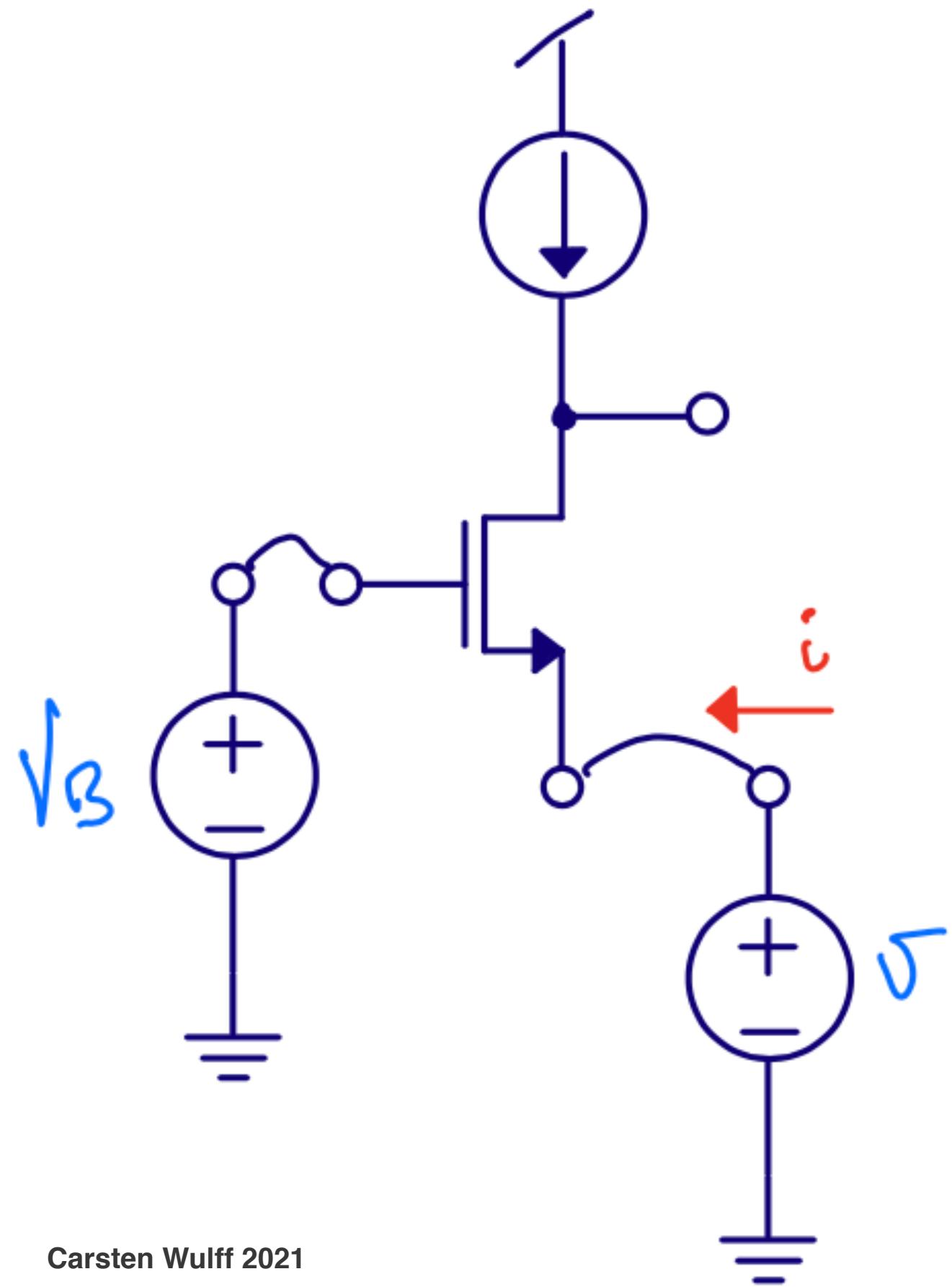

Input resistance ?

Gain ?

Output resistance ?

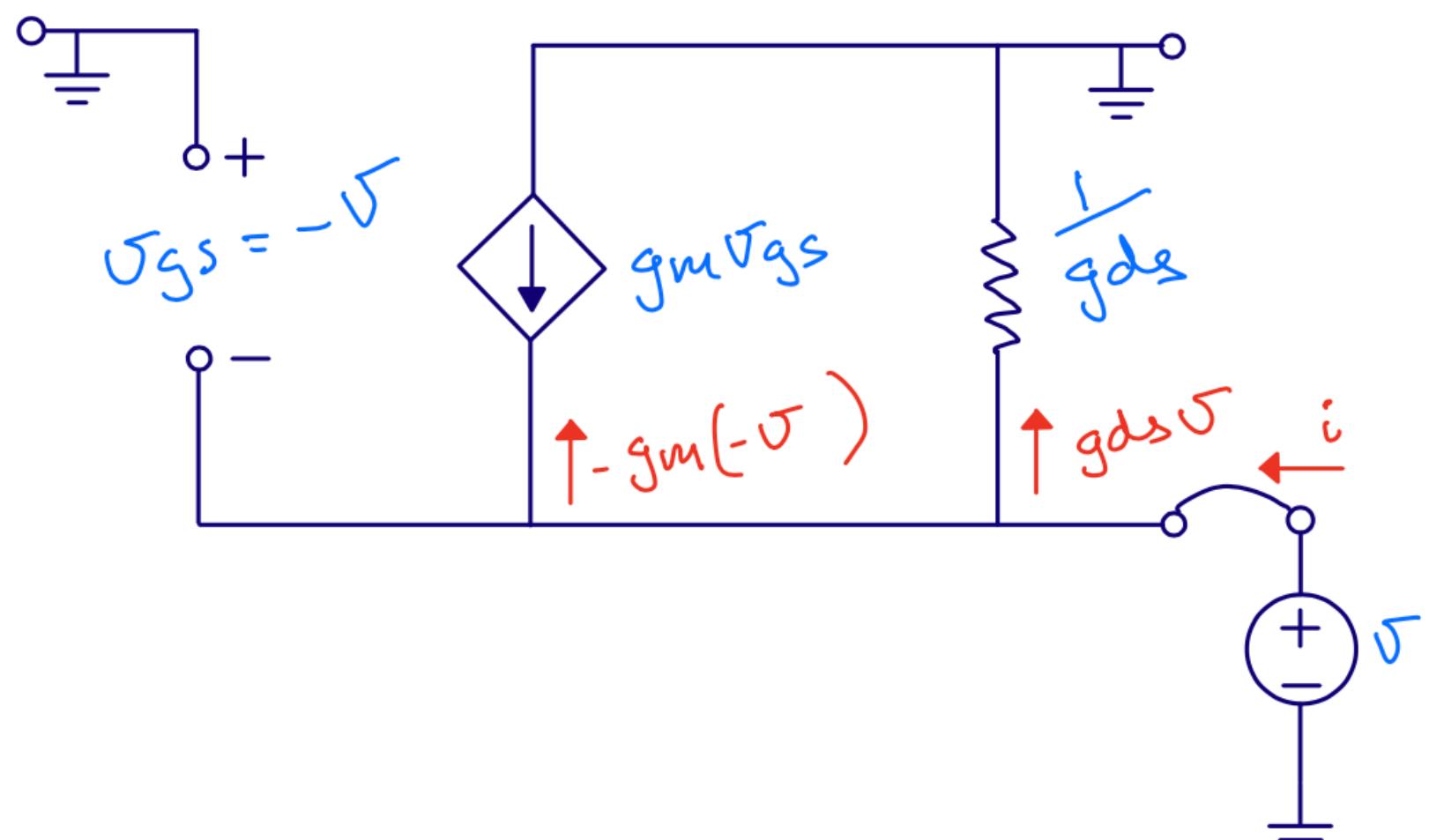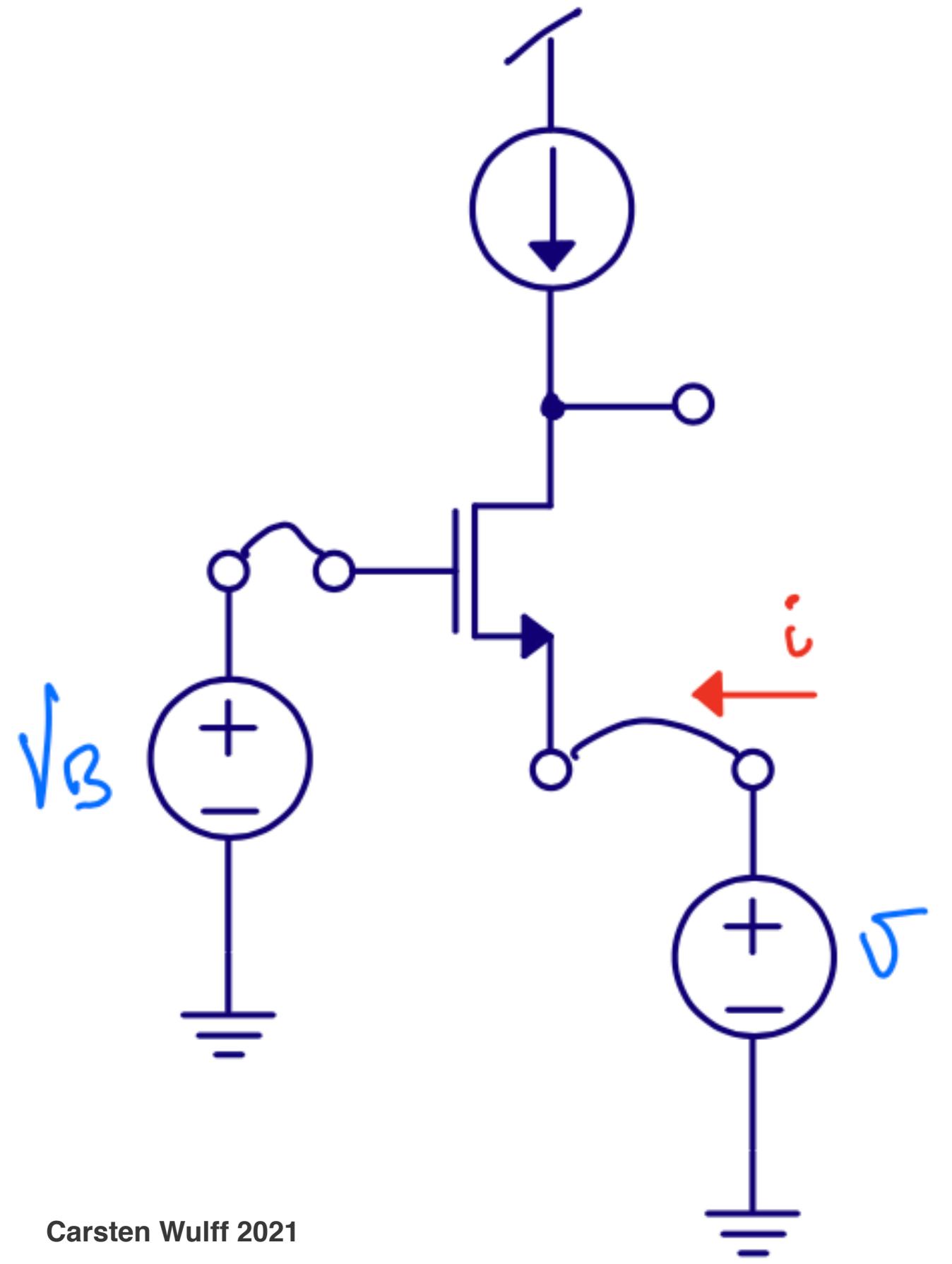


Common gate - r_{in}


$$i = g_m v + g_{ds} v$$

$$r_{in} = \frac{1}{g_m + g_{ds}} \approx \frac{1}{g_m}$$



However, we've ignored load resistance.
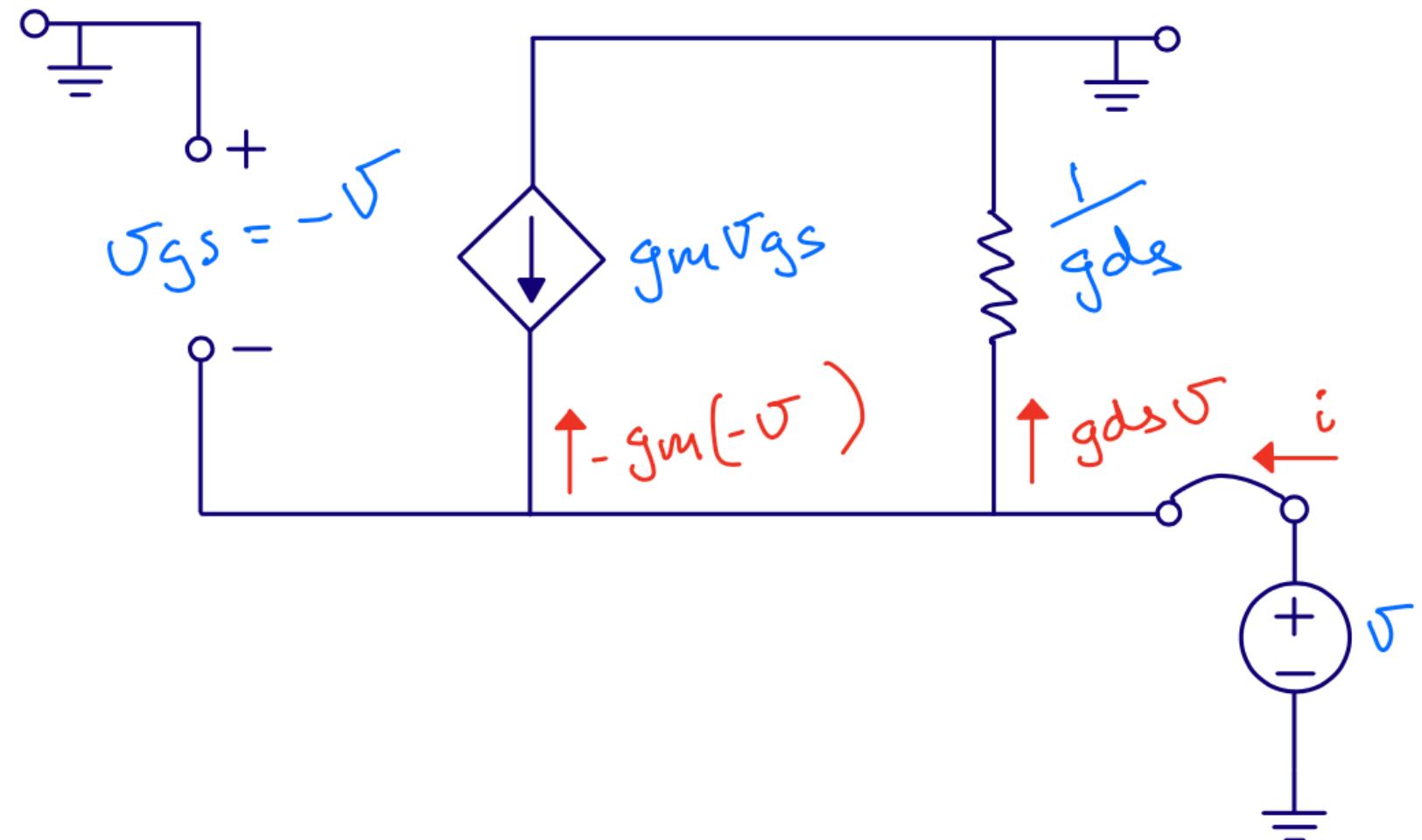
$$r_{in} \approx \frac{1}{g_m} \left(1 + \frac{R_L}{r_{ds}} \right)$$



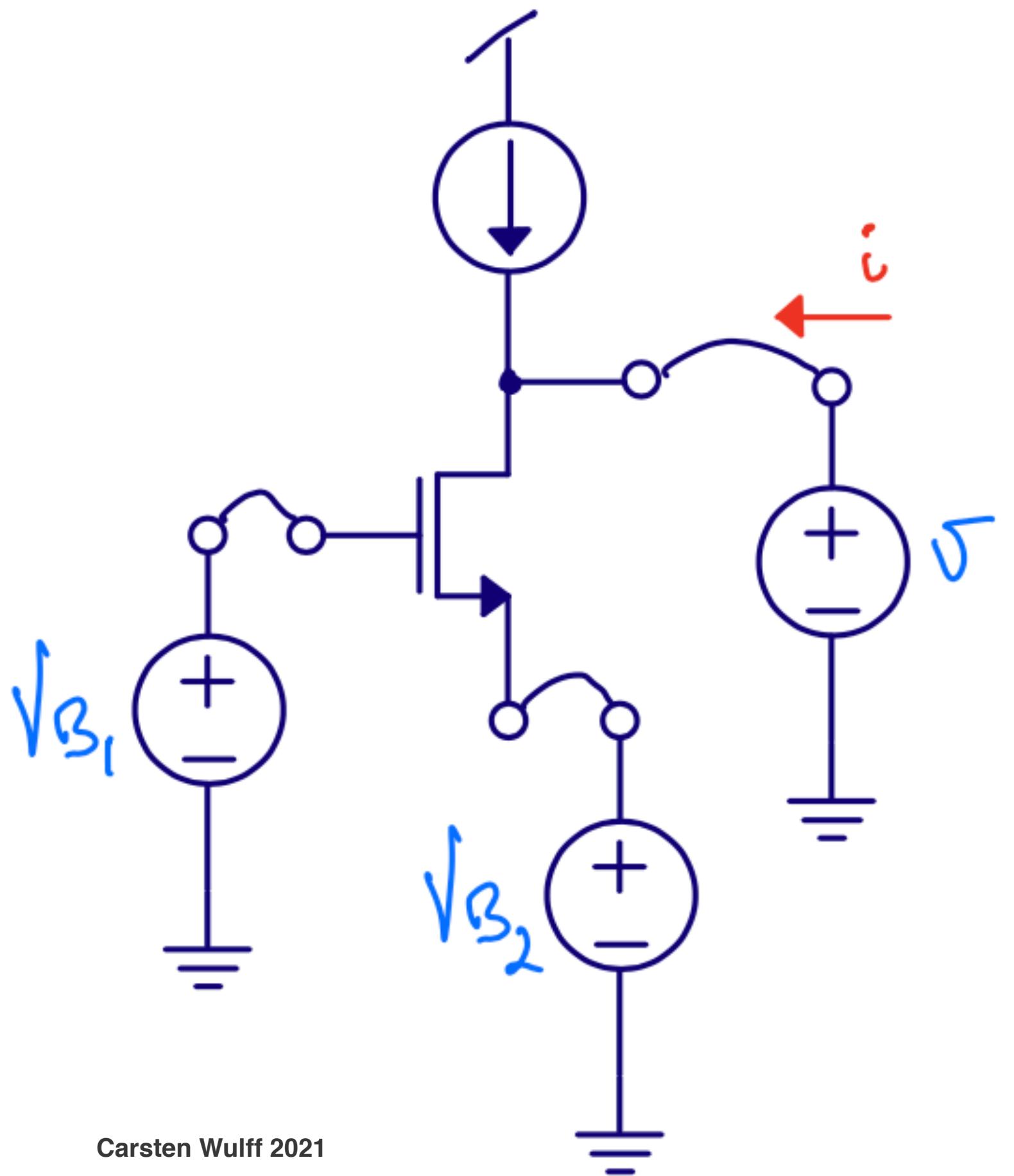



Common gate - r_{out}

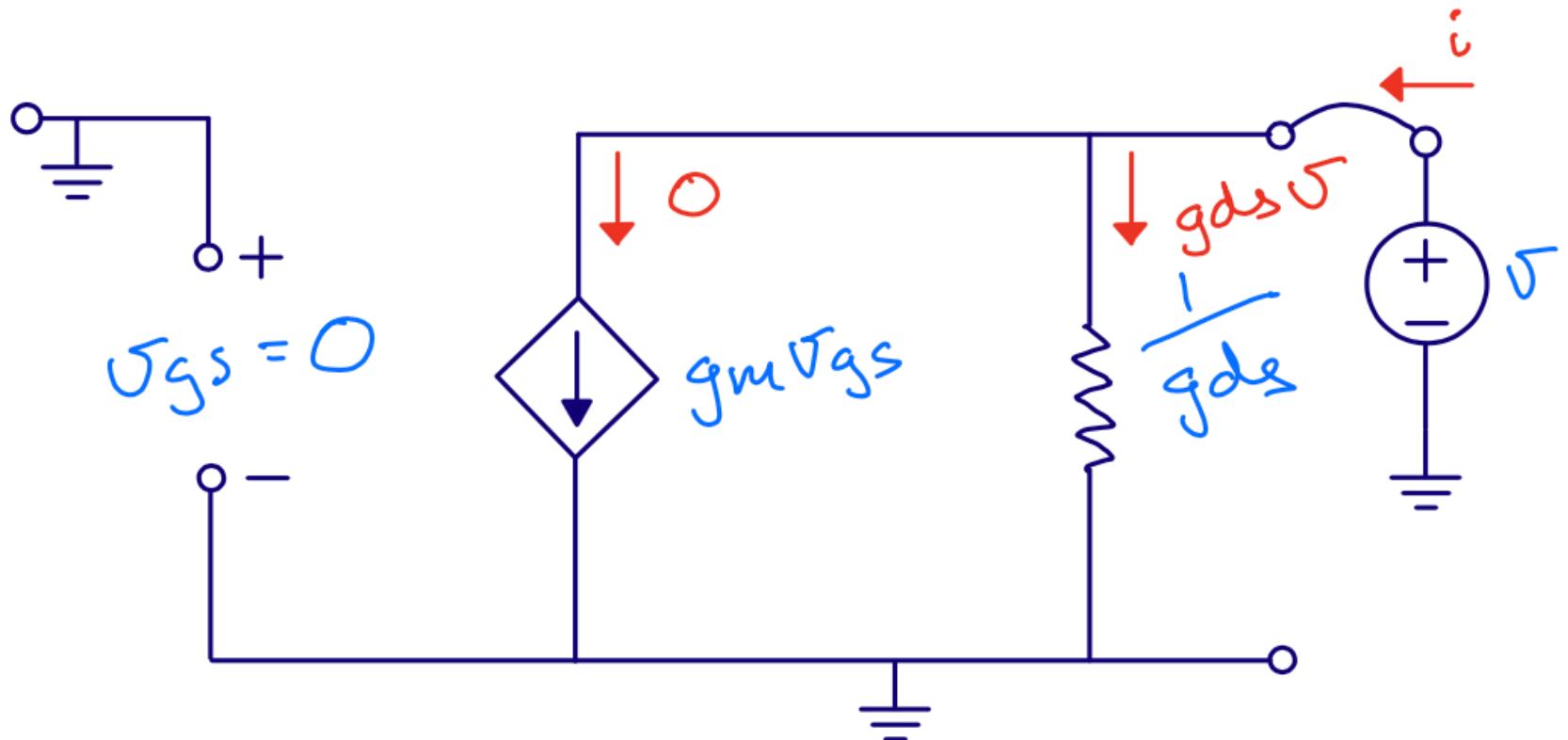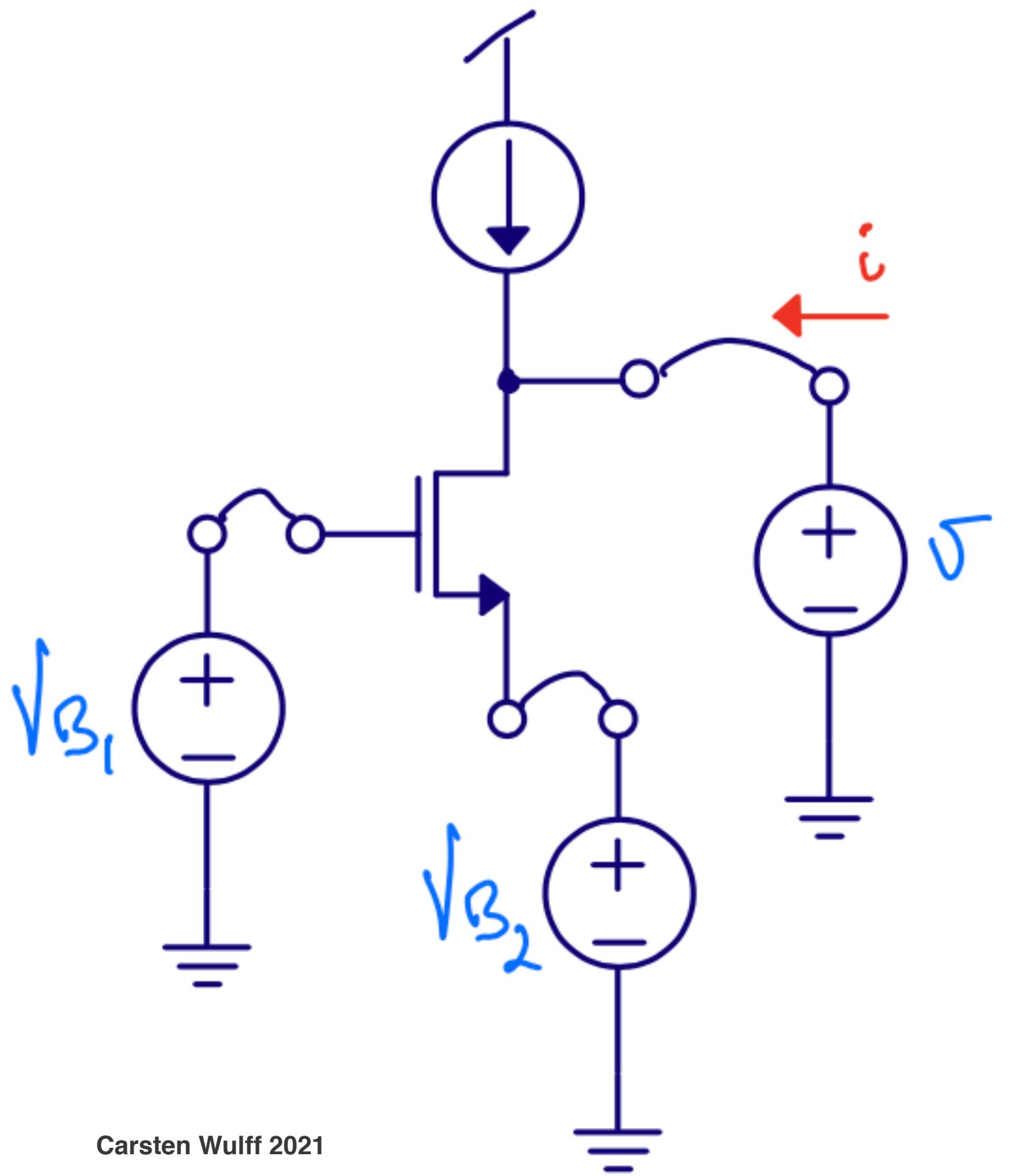



Common gate - r_{out}

$$r_{out} = r_{ds}$$

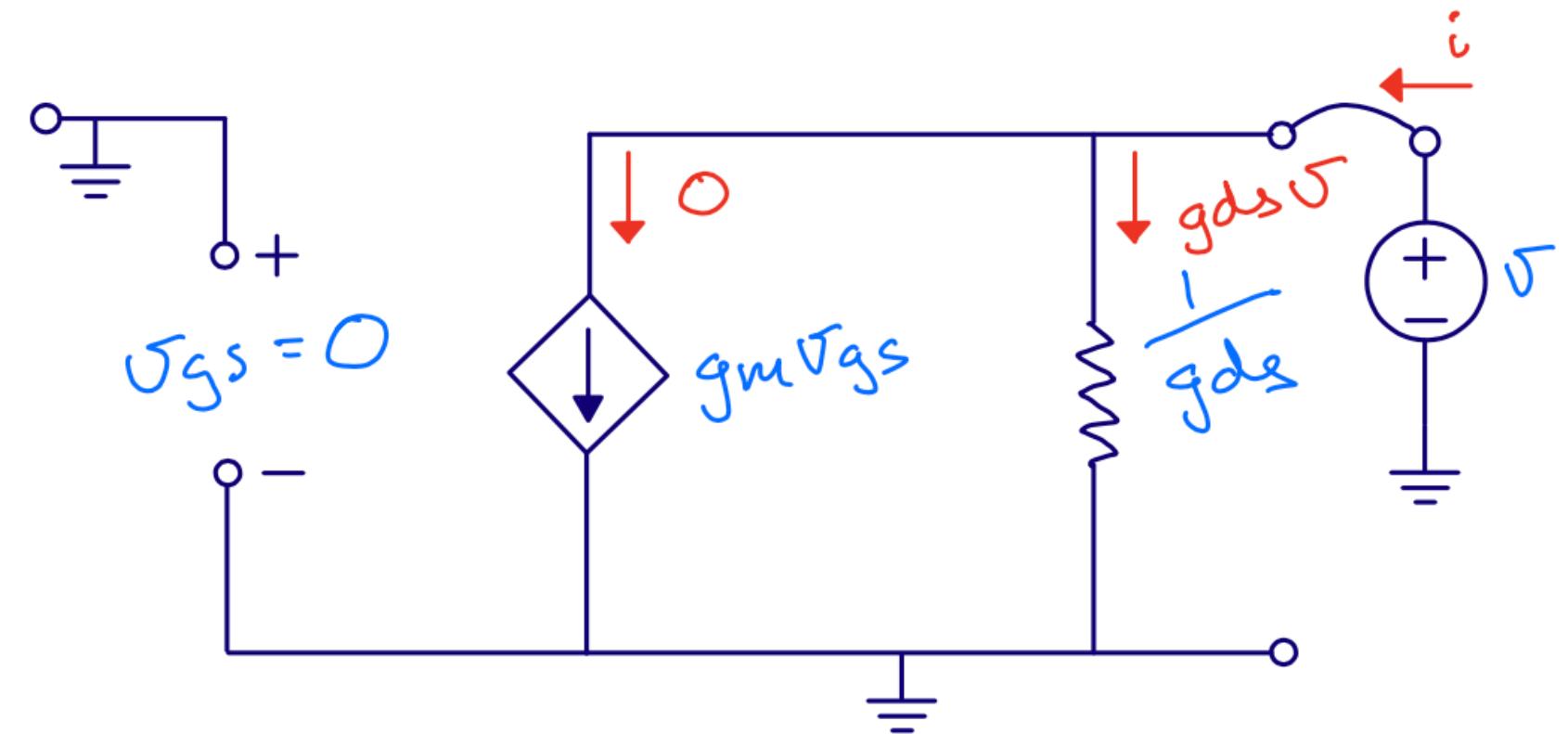

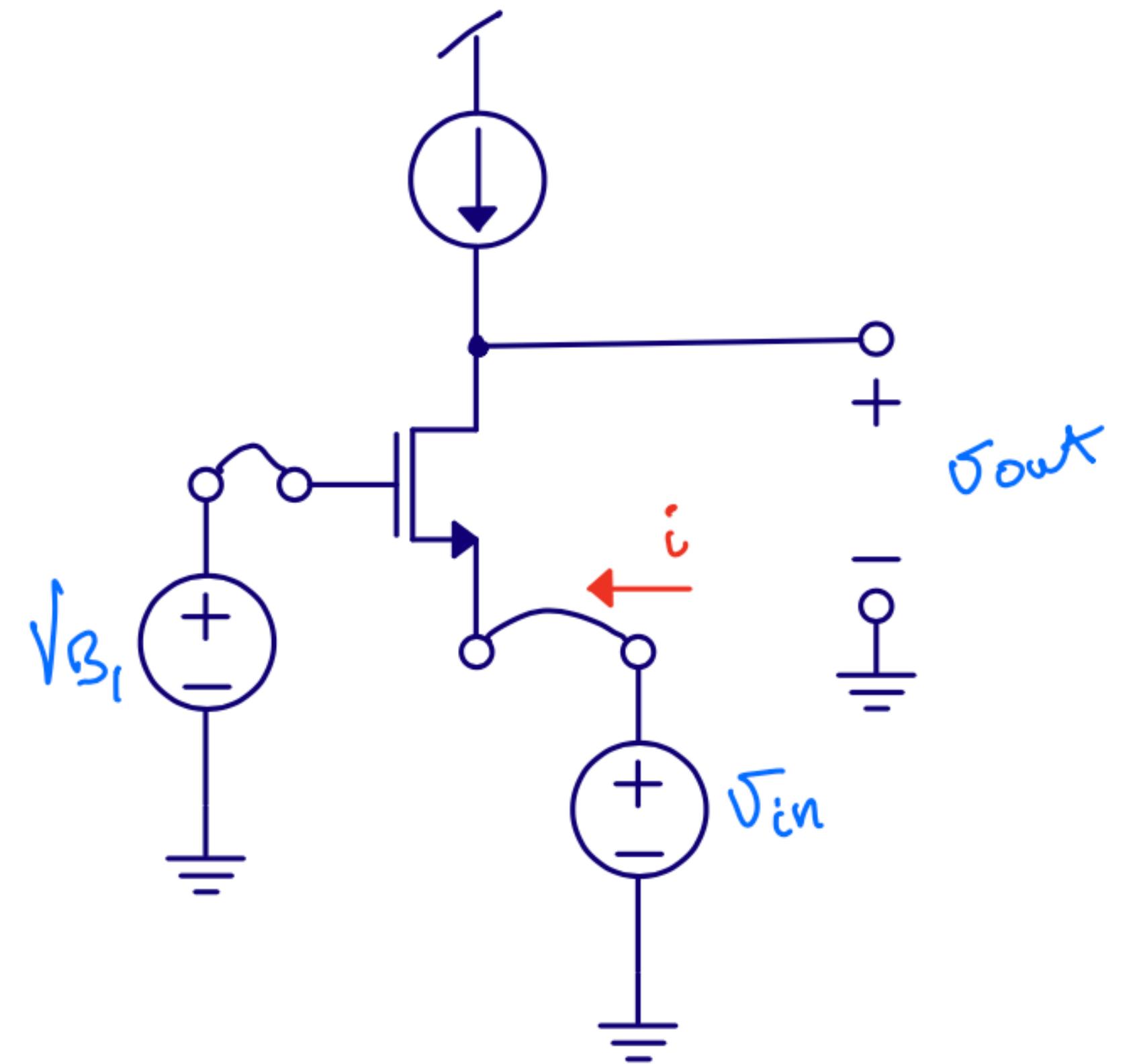

Common gate -
Gain

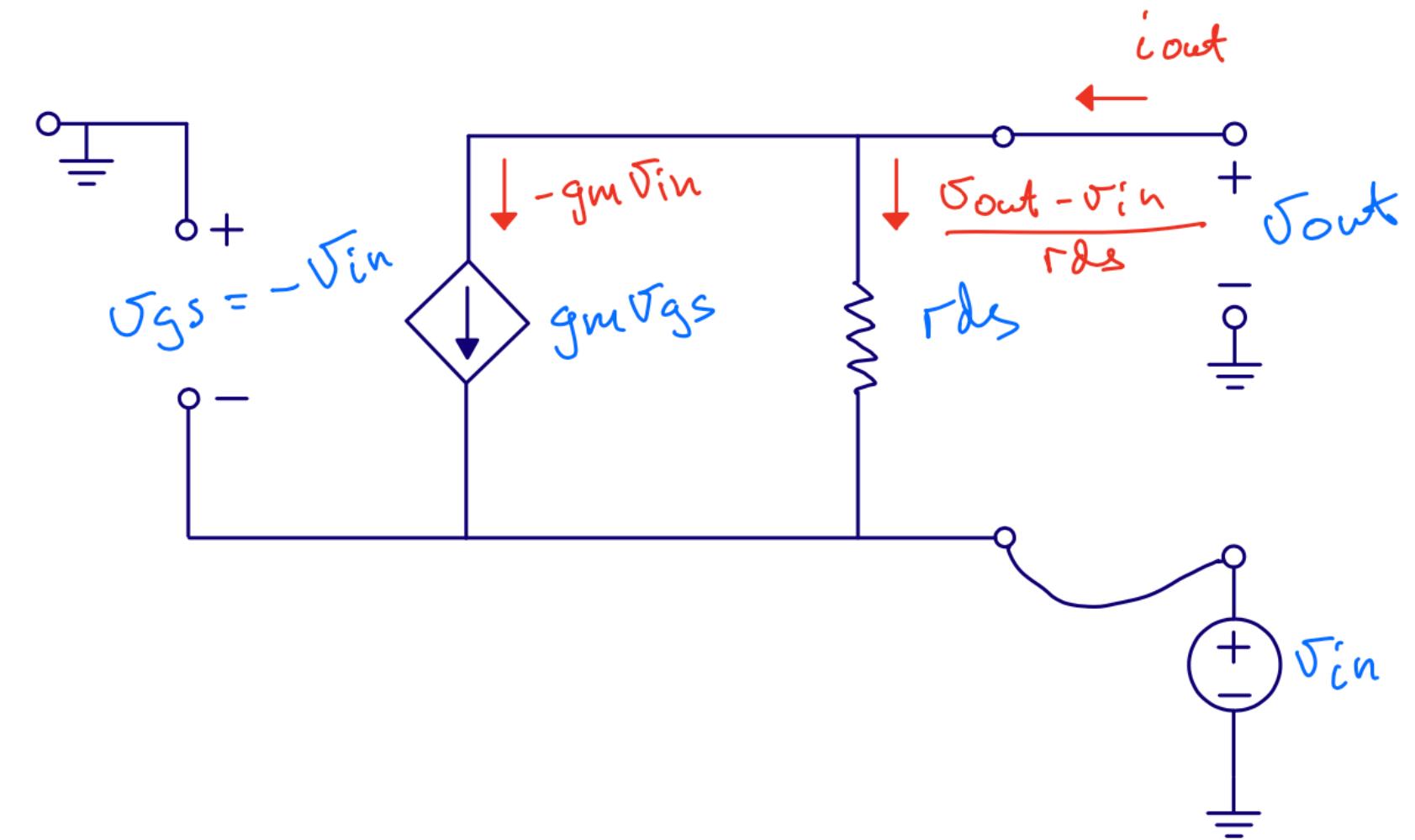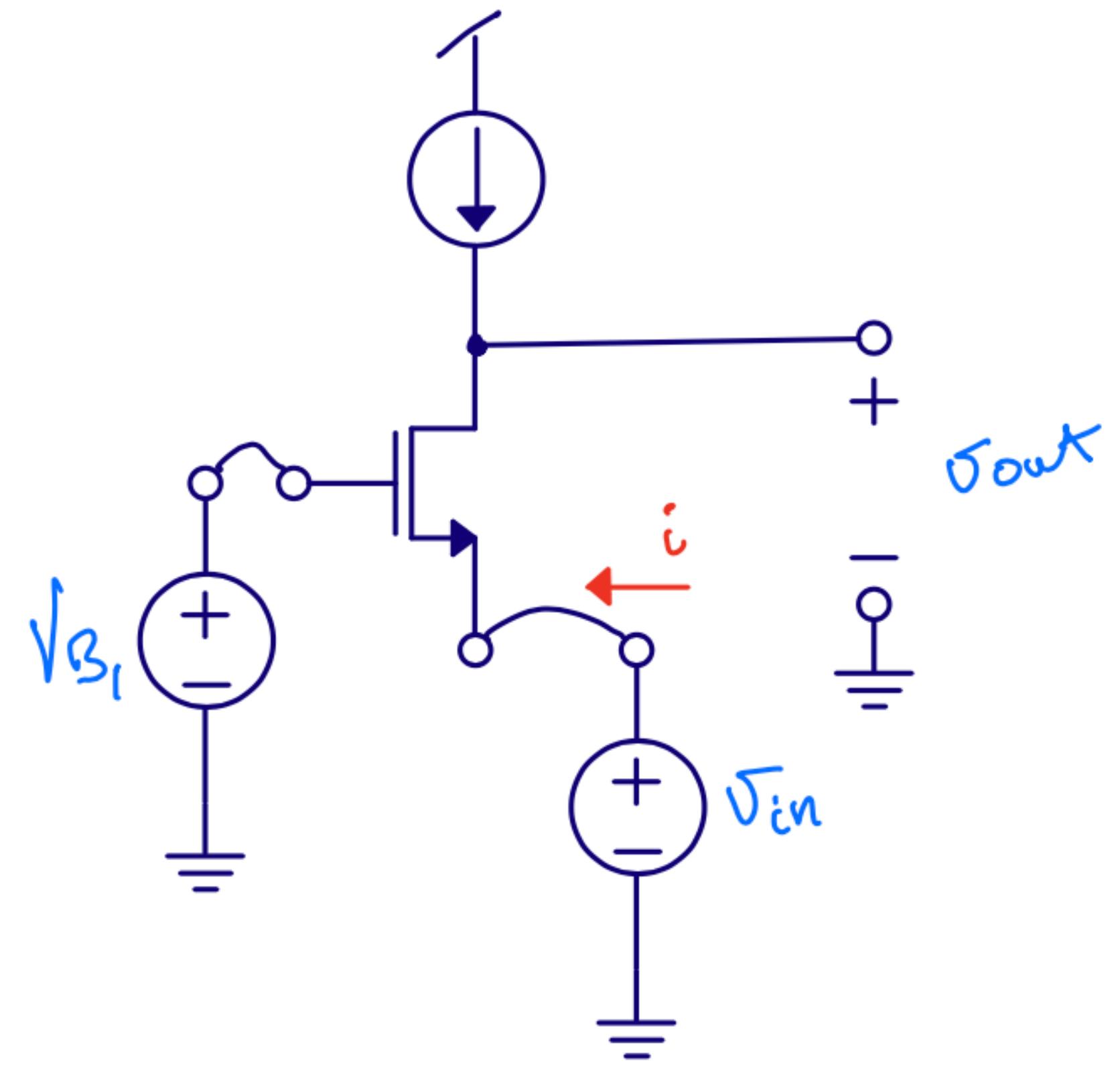

Common gate - Gain


$$i_o = -g_m v_i + \frac{v_o - v_i}{r_{ds}}$$

$$i_o = 0$$

$$0 = -g_m v_i r_{ds} + v_o - v_i$$

$$v_i (1 + g_m r_{ds}) = v_o$$

$$\frac{v_o}{v_i} = 1 + g_m r_{ds}$$

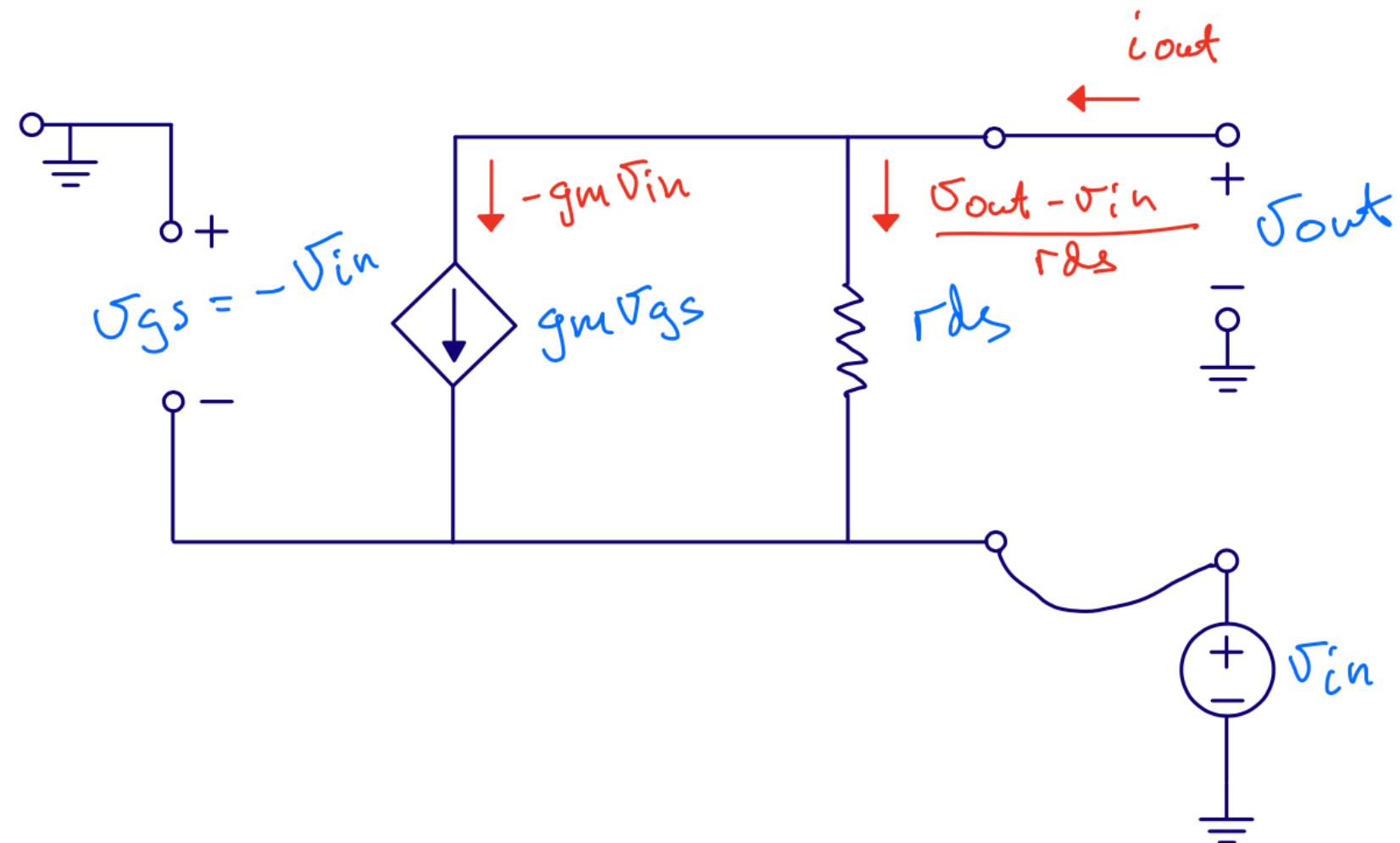


Common gate - Gain

We've ignored bulk effect (g_s), source resistance (R_S) and load resistance (R_L)

$$A = \frac{(g_m + g_s + g_{ds})(R_L || r_{ds})}{1 + R_S \left(\frac{g_m + g_s + g_{ds}}{1 + R_L / r_{ds}} \right)}$$


If $R_L \gg r_{ds}$, $R_S = 0$ and $g_s = 0$
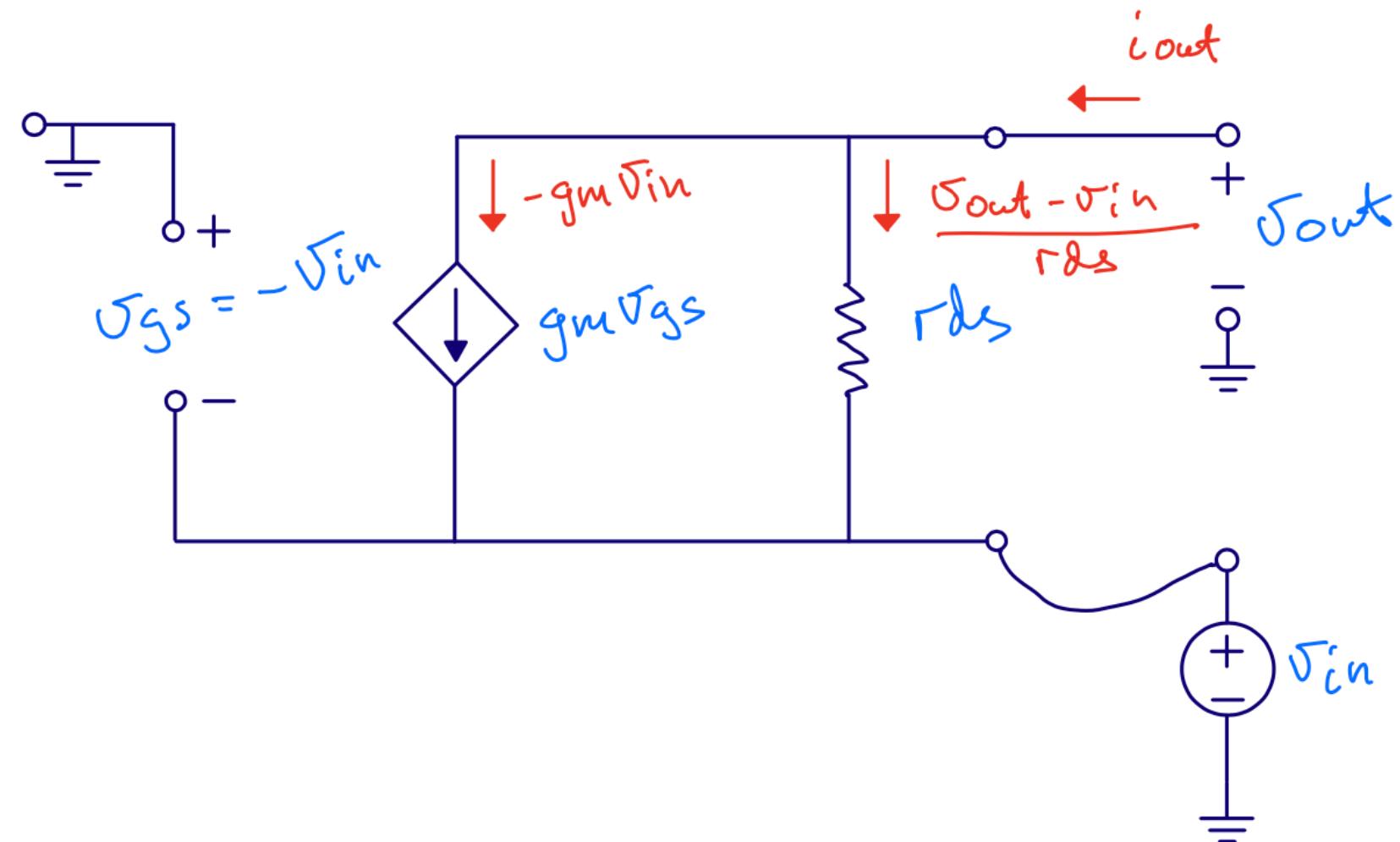
$$A = \frac{(g_m + g_{ds})r_{ds}}{1} = 1 + g_m r_{ds}$$



Common source



Common source

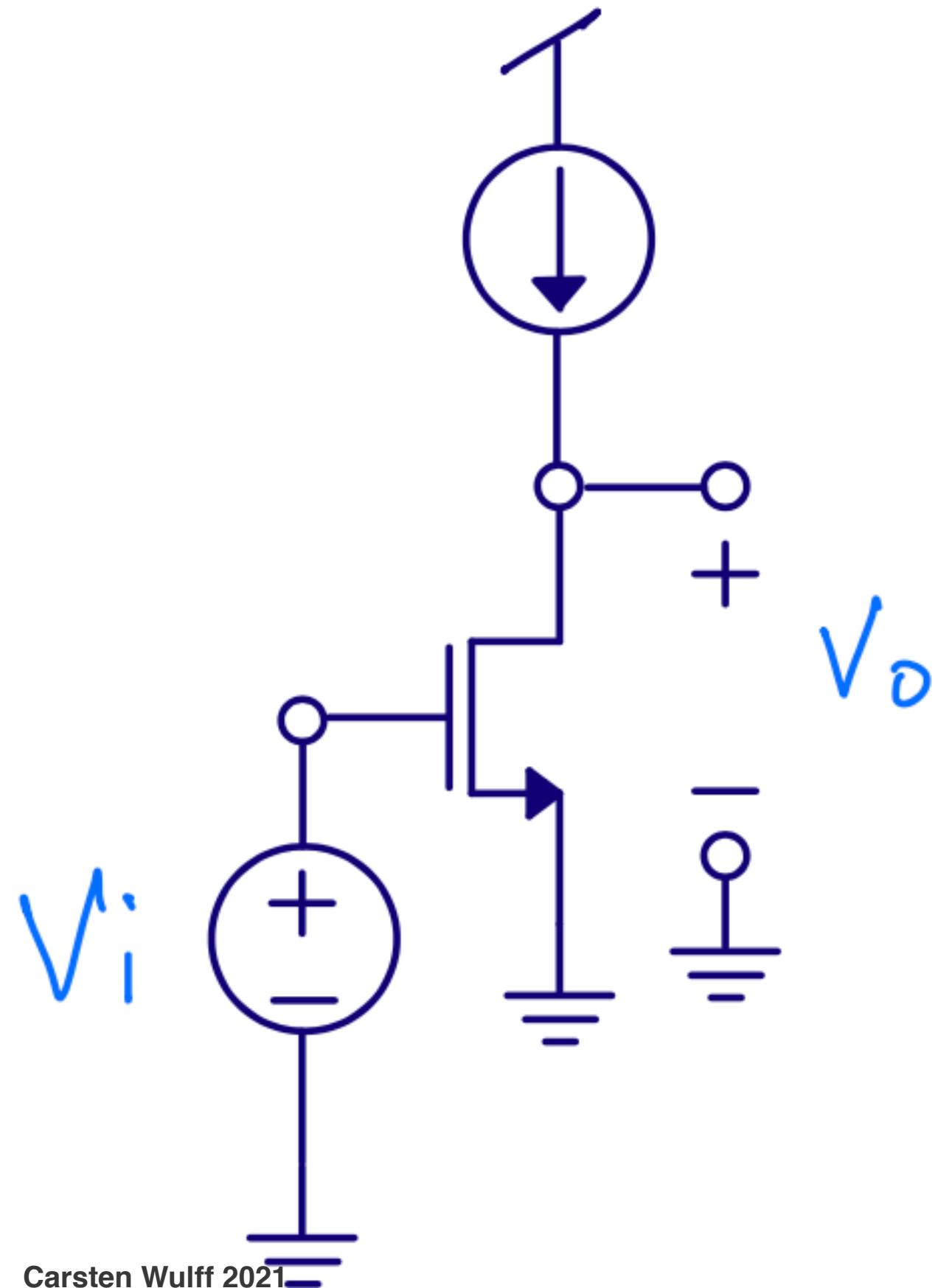

Input resistance $r_{in} \approx \infty$

Output resistance $r_{out} = r_{ds}$, it's same circuit as the output of a current mirror

Gain ?

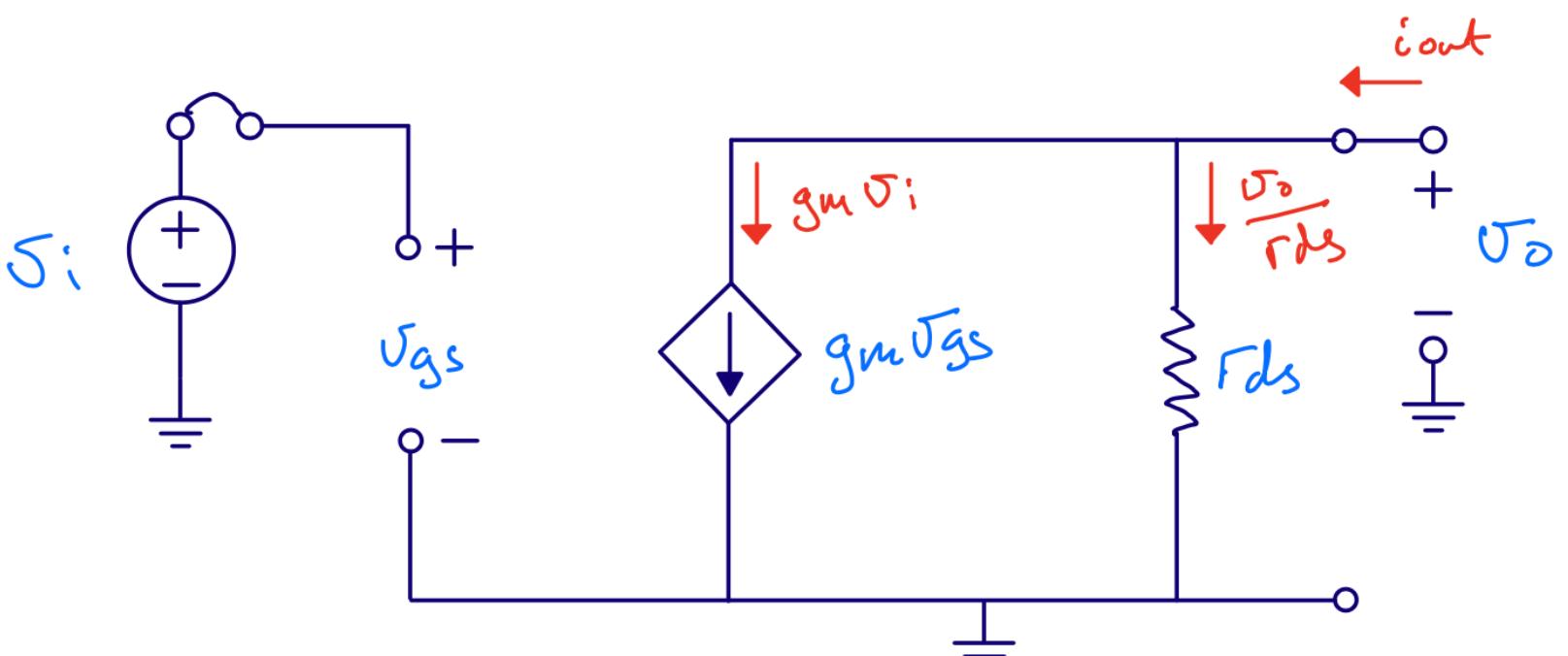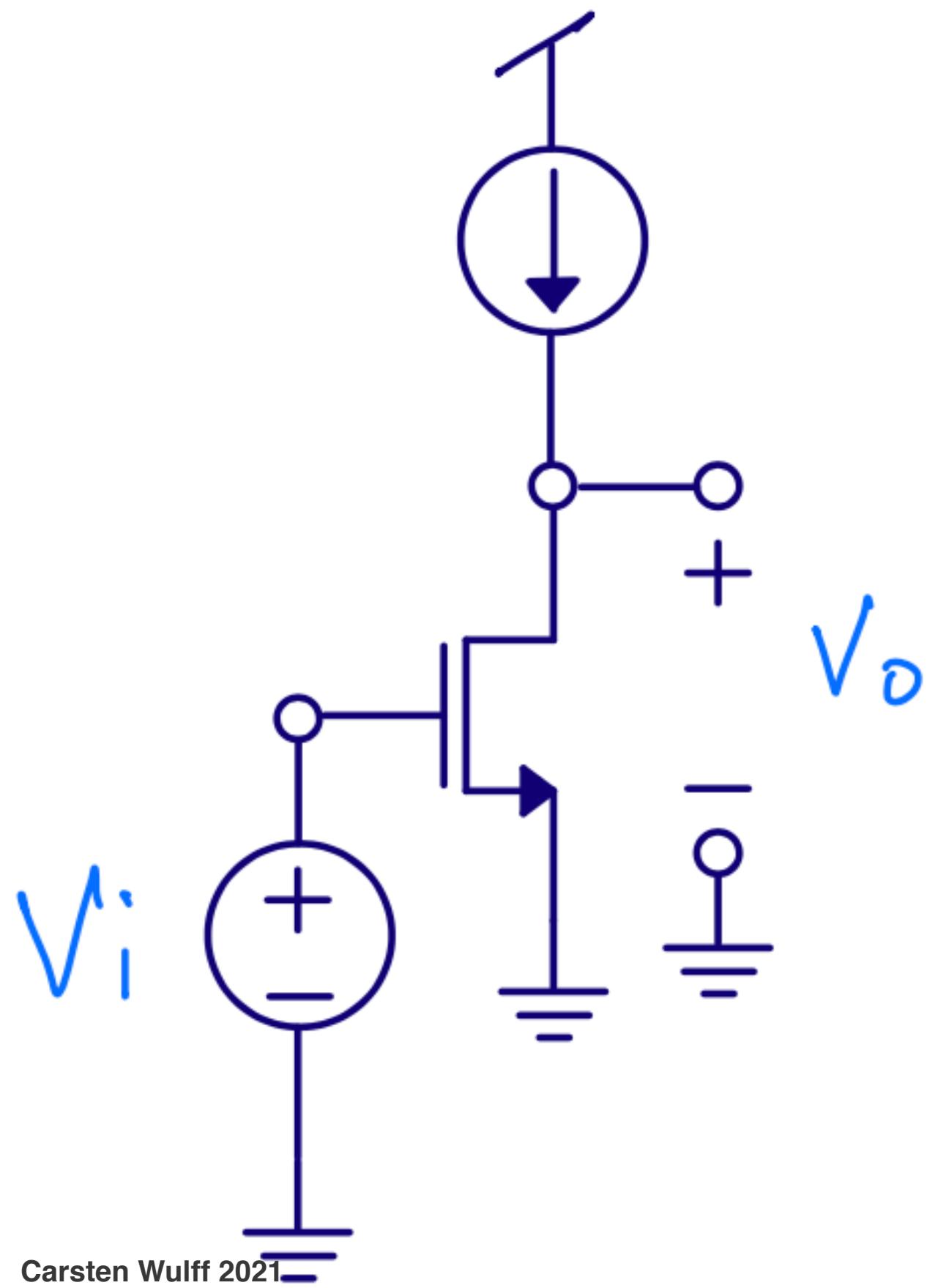


Common source - Gain


$$i_o = g_m v_i + \frac{v_o}{r_{ds}}$$

$$i_o = 0$$


$$-g_m v_i = \frac{v_o}{r_{ds}}$$

$$\frac{v_o}{v_i} = -g_m r_{ds}$$

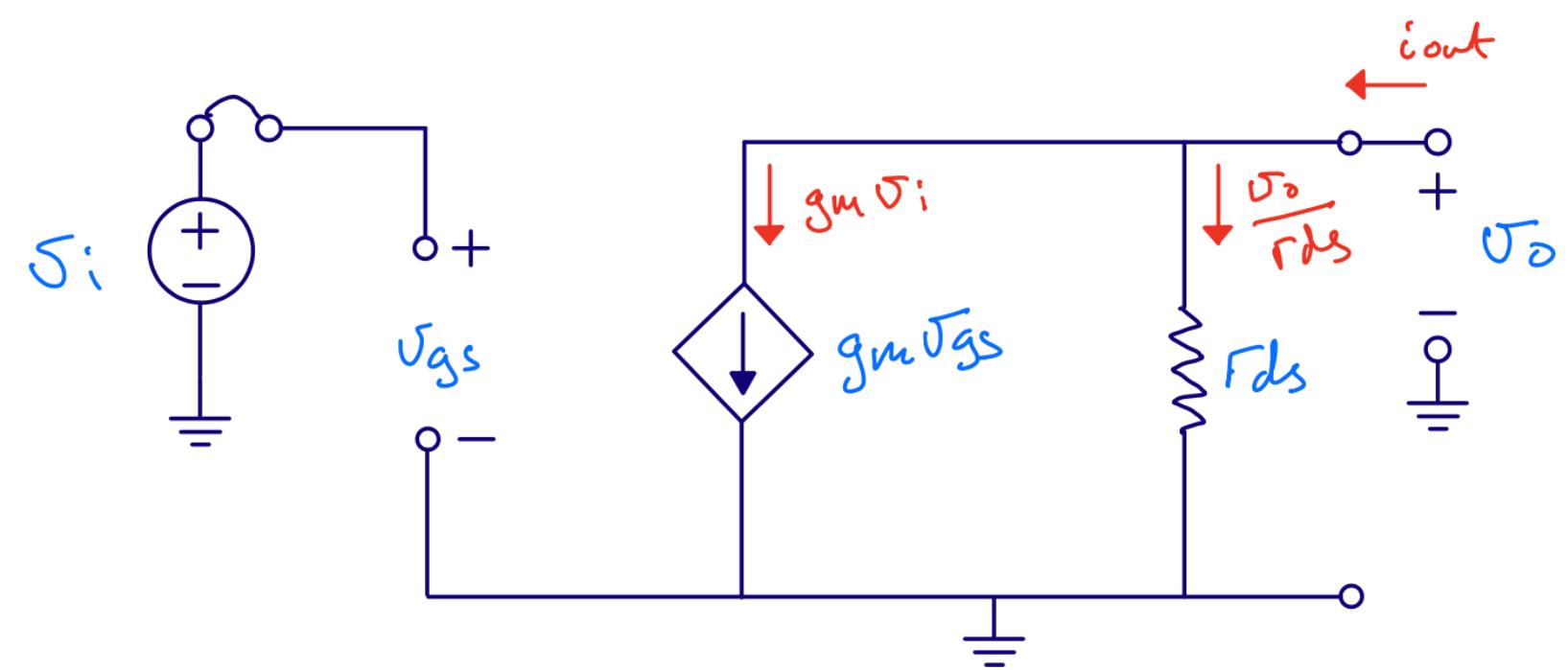

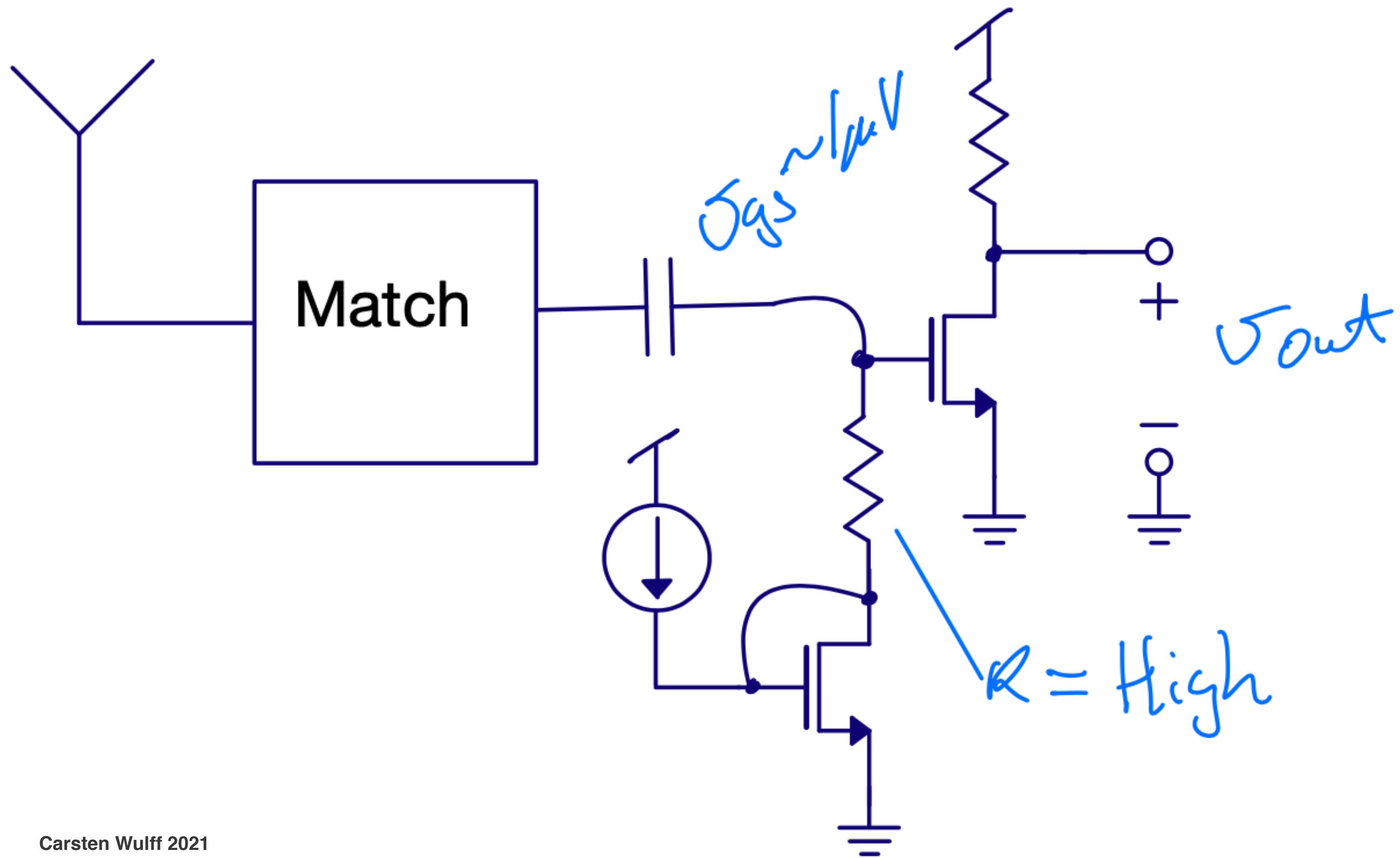

Differential pair

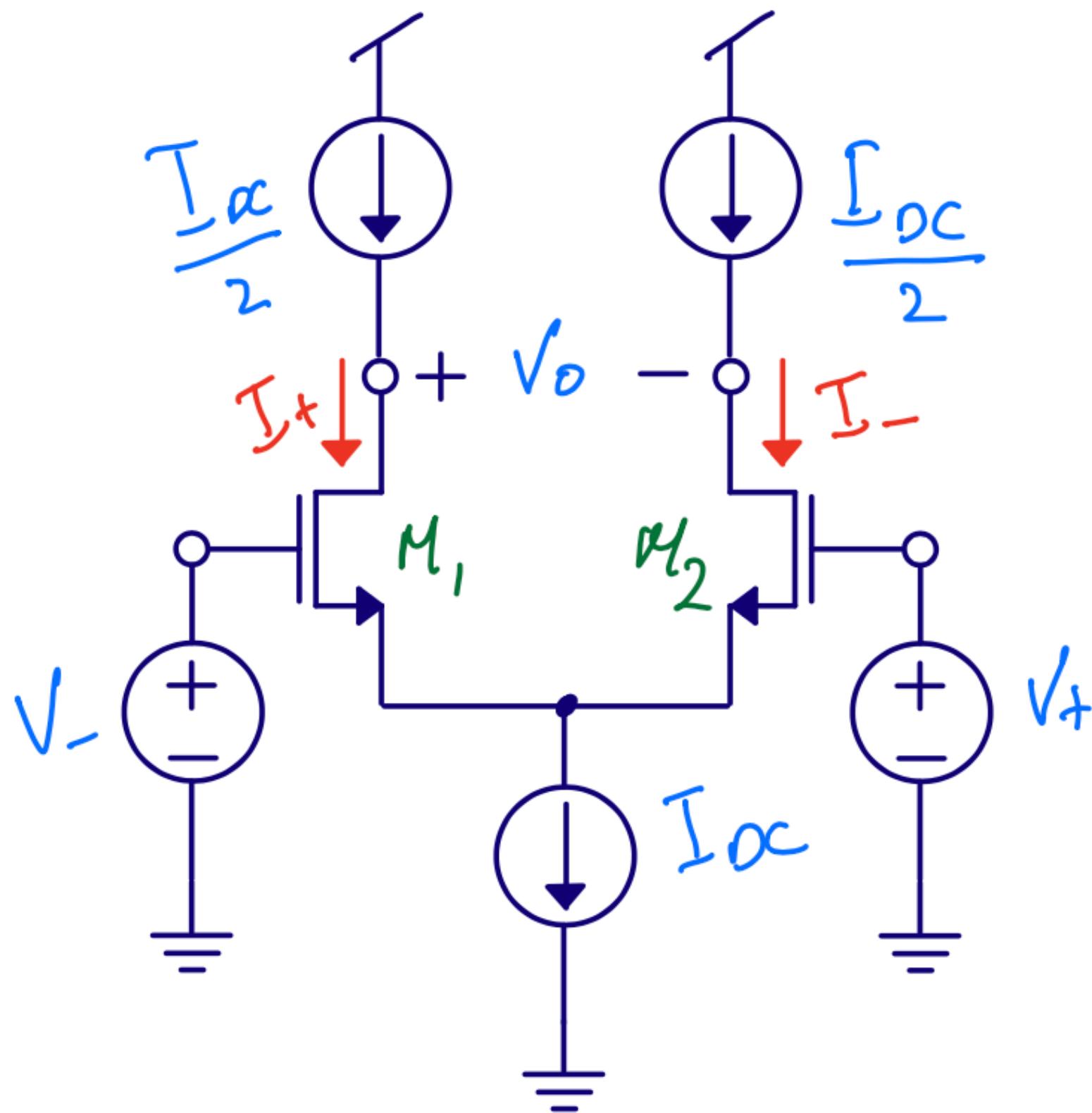

Input resistance $r_{in} \approx \infty$

Gain $A = g_m r_{ds}$

Output resistance $r_{out} = r_{ds}$

Best analyzed with T model of transistor
(see CJM page 31)

Diff pairs are cool


Can choose between


$$v_o = g_m r_{ds} v_i$$

and

$$v_o = -g_m r_{ds} v_i$$

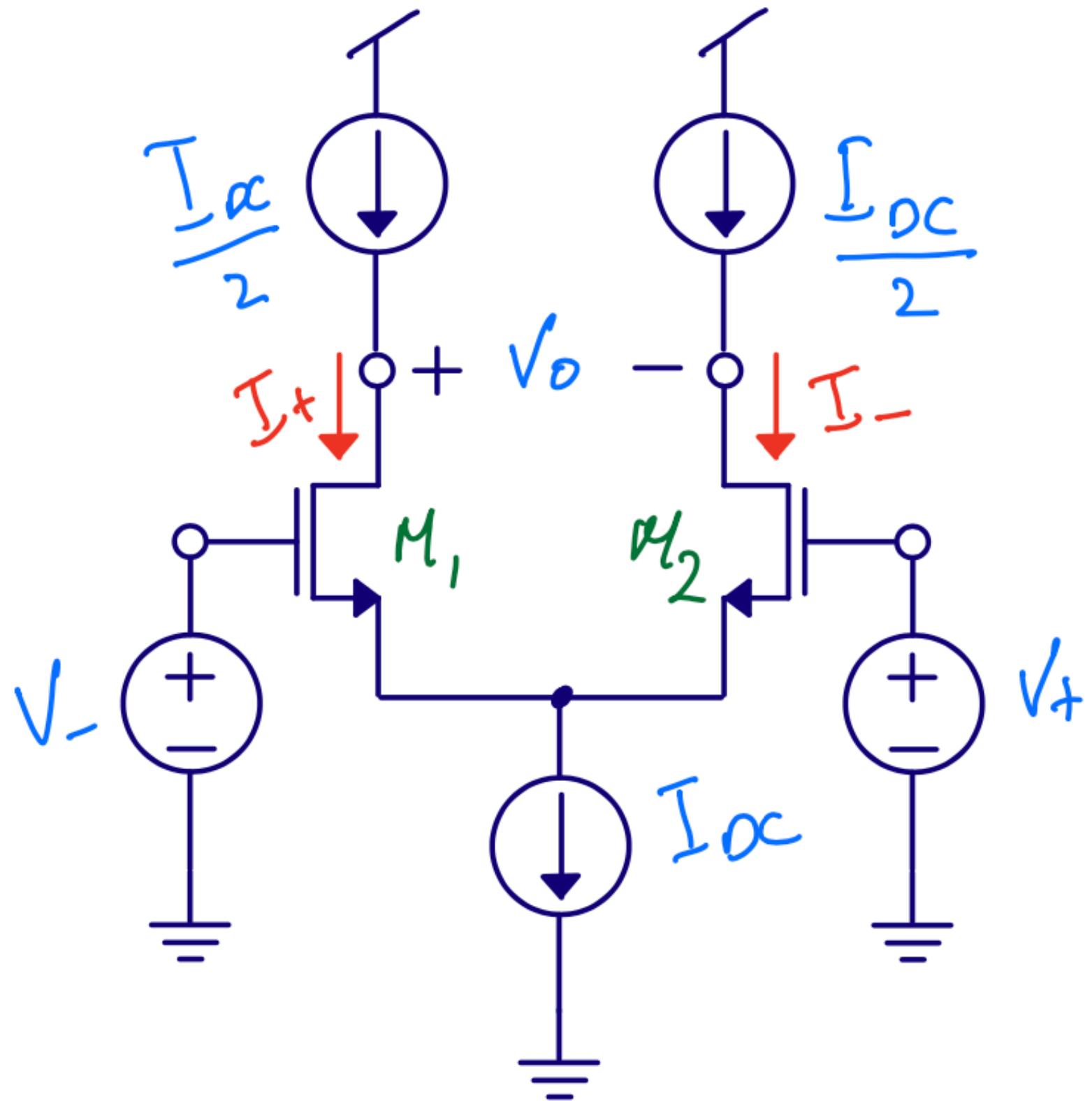by flipping input (or output) connections



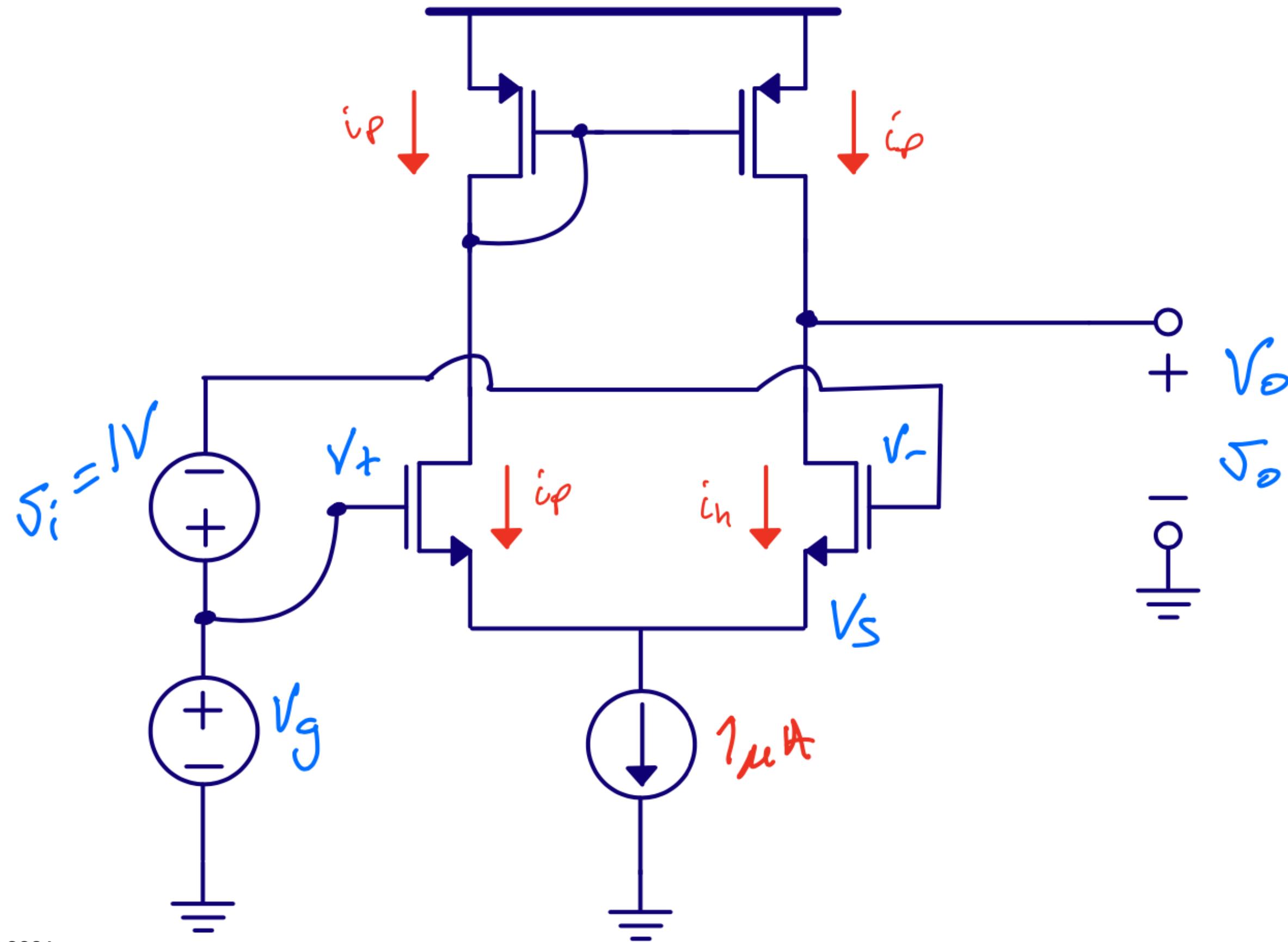

Thanks!

